

MOSFET FIGURES OF MERIT

(1)

Let's consider a MOSFET n-type with source and drain shorted to ground while the gate is biased at $V_G > V_T$. The drain is biased with $V_D > 0$. In the channel we have


$$dV_C = I_{DS} \cdot dR = I_{DS} \cdot \frac{dx}{q m \mu_m W \Delta} = I_{DS} \cdot \frac{dx}{Q_m(x) \mu_m W}$$

where $Q_m(x) = C_{ox} (V_G - V_C - V_T)$

$$\int_{V_{DS}}^{V_{DS}} W \mu_m C_{ox} (V_G - V_C - V_T) dV_C = \int_0^L I_{DS} dx$$

$$I_{DS} = \mu_m C_{ox} \frac{W}{L} \left[(V_G - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$$
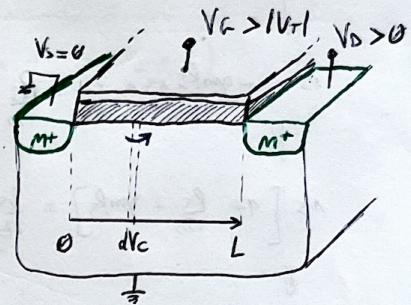
$$I_{DS}^{SAT} = \frac{1}{2} \mu_m C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$



For V_{DS} values $> V_{DS}^{SAT} = (V_{GS} - V_T)$, the previous relation is no longer valid. At steady state the current along the source is equal to the one reaching the drain side, so the drift velocity (and the electric field) must increase as we move towards the drain, since $m \downarrow$ and $\mu \cdot m \cdot v \approx \text{constant}$. In the point called PINCH-OFF we have $Q'_m = 0$ (negligible) and it is expected to increase downwards as V_{DS} increases above V_{DS}^{SAT} , which in the area behind the pinch-off point the previous relation is still valid, so

$$I_{DS}^{SAT'} = k' \frac{W}{L'} (V_G - V_T)^2 \quad [k' = \frac{1}{2} \mu_m C_{ox}]$$

when $L' < L$, $\Rightarrow I_{DS}^{SAT'} > I_{DS}^{SAT}$. Assuming that $(L - L')$ remains small, as suggested by the operating I-V curves, we get that

$$I_{DS} = I_{DS}^{SAT} + \left(\frac{\partial I_{DS}}{\partial V_{DS}} \right) \Big|_{V_{DS}=V_{DS}^{SAT}} \cdot (V_{DS} - V_{DS}^{SAT})$$

where

$$\frac{\partial I_{DS}}{\partial V_{DS}} = \frac{\partial I_{DS}^{SAT}}{\partial L} \frac{\partial L}{\partial V_{DS}^{SAT}} = - \frac{I_{DS}^{SAT}}{L} \cdot \frac{\partial L'}{\partial V_{DS}} \Big|_{V_{DS}=V_{DS}^{SAT}}$$

$$\therefore I_{DS} = I_{DS}^{SAT} \left[1 + \lambda (V_{DS} - V_{DS}^{SAT}) \right] \quad (\lambda = - \frac{1}{L} \frac{\partial L'}{\partial V_{DS}} \Big|_{V_{DS}=V_{DS}^{SAT}})$$

We define $\frac{1}{\lambda} = V_A$ EARLY VOLTAGE.

Does not depend on current!

→ GAIN

The maximum gain of a MOSFET is $gm_{zo} = \mu = \frac{2I}{V_{AO}} \cdot \frac{V_A}{I} = \frac{2V_A}{V_{AO}}$

$$V_A = \frac{V_{DS}}{1 + \frac{V_{DS}}{V_{AO}}}$$

②

→ RESISTANCES

• (R_D)

$$v_o = i_s \cdot R_s$$

$$i_s = -g_m v_o + \frac{v_s - v_o}{R_o}$$

↓


$$i_s = -g_m R_s i_s + \frac{v_s}{R_o} - \frac{R_s}{R_o} i_s$$

↓

$$i_s \left[1 + \frac{R_s}{R_o} + g_m R_s \right] = \frac{v_s}{R_o}$$

↓
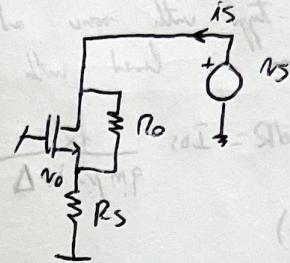
$$\frac{v_s}{i_s} = R_o + R_s + g_m R_s r_o = R_o + R_s \left[1 + g_m r_o \right]$$



• (R_S)

$$v_o = i_s \cdot R_s$$

$$i_s = g_m v_i + \frac{v_s - v_o}{R_o}$$

↓


$$i_s = -\frac{R_s}{R_o} i_s + \frac{v_i}{R_o} + g_m v_i$$

↓

$$v_i \left[g_m + \frac{1}{R_o} \right] = i_s \left[1 + \frac{R_s}{R_o} \right]$$

↓
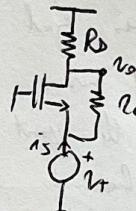
$$\frac{v_i}{i_s} = \frac{1 + \frac{R_s}{R_o}}{1 + g_m} = \frac{R_o + R_s}{1 + g_m R_o}$$



→ WEAK INVERSION

In this regime electrons are not density the electric field in the channel, so the fields are almost flat. The conduction of electrons at the same rate is ensured by using the M-B statistics

$$M(O) = N_s \cdot e^{-\frac{q \phi_B}{kT}}$$

big $\phi_B = V_{DD} - \psi_s$. The current is due to diffusion!

$$J_m = q D_m \frac{dm}{dx} = q D_m \frac{M(O)}{L} = q D_m \frac{N_s^2}{L N_A} \cdot \frac{q \psi_s}{k T}$$

It can be shown that

$$I_{DS} = 4m \left(\frac{1}{2} \mu_{n,s} C_{ox} V_{TH}^2 \right) \cdot \frac{q (V_{DD} - V_T)}{k T}$$

$$(m = 1 + \frac{C_{ox}}{C_{par}} \approx 1,5)$$

$$\approx \frac{2 I_{DS}}{2 V_{DD}} = g_m = \frac{I_{DS}}{m V_{TH}} \quad \text{and} \quad \mu = g_m r_o = \frac{V_o}{m V_{TH}}$$

→ Moderate Inversion

EKV model

$$I_C = \frac{I_D}{4m \left[\frac{1}{2} \mu m C_{ox} \frac{W}{L} (V_{TH})^2 \right]}$$

$$g_m = \frac{2}{1 + \sqrt{1 + 4 \cdot IC}} \quad \frac{I_D}{m V_{TH}}$$

TAKEN BY	IC	BIAS RANGE
WEAK Inv.	$IC \leq 0,1$	$V_{BS} \geq V_{TH} - 0,1V$
Moderate Inv.	$0,1 \leq IC \leq 10$	$ V_{TH} - 0,1V \leq V_{BS} \leq V_{TH} + 0,2V$
STRONG Inv.	$IC \geq 10$	$V_{BS} \geq V_{TH} + 0,2V$

$$\left(M = 1 + \frac{C_{DS}}{C_{ox}} = 1,5 \right)$$

→ Cut-Off Frequency

Frequency for a unity current gain

$$\frac{i_{out}}{i_S} = g_m R_L$$

$$f_T = \frac{1}{2\pi} \frac{1}{R_L \cdot C_o}$$

||

$$f_T = g_m R_L \cdot \frac{1}{2\pi C_o \cdot R_L} = \frac{g_m}{2\pi C_o}$$

Assuming that $C_o = C_{gs} \approx C_{ox} \cdot W/L$ then

$$f_T \approx \frac{2 \cdot \frac{1}{2} \mu m C_{ox} \frac{W}{L} V_{DD}}{2\pi C_{ox} W/L} = \frac{1}{2\pi} \frac{\mu m F}{L} = \frac{1}{2\pi} \frac{2}{L} = \frac{1}{2\pi} \frac{1}{2\text{DRIFT}}$$

In weak inversion instead, we have that


$$Q' = \frac{q}{2} \cdot m(o) \cdot L \quad [\text{charge per unit area}]$$

$$J_m = q D_m \frac{m(o)}{L} \quad [\text{current density}]$$

$$2\text{DRIFT} = \frac{Q'}{J_m} = \frac{L^2}{2 D_m}$$

$$\text{and } f_T = \frac{1}{2\pi 2\text{DRIFT}}$$
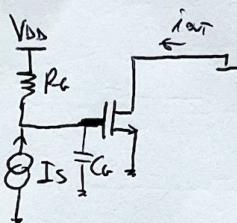
$$2\text{DRIFT} < 2\text{DIFF} \Rightarrow \frac{L^2}{\mu m V_{DD}} < \frac{L^2}{2 D_m} \Rightarrow V_{DD} > 2 \frac{\mu m W}{\mu m 9} = 2 V_{TH}$$



QUANTITATIVE DESCRIPTION OF NOISE

Main noise constraints on the minimum current value. We can split any signal into

$$y(t) = \underbrace{s(t)}_{\text{INFORMATION}} + \underbrace{n(t)}_{\text{NOISE}} + \underbrace{d(t)}_{\text{DISTORTION}}$$

↓ ↓ ↓

USEFUL UNAVOIDABLE AVOIDABLE

We'll consider Gaussian noise (gaussian amplitude distribution), with zero mean value and power σ^2 time-invariant. We consider σ as a reference value to study noise fluctuations. Moreover, we consider ERGODIC noise, where time average is related equal to the ensemble average. In general, noise, like signals, can be described as the superposition of orthogonal harmonics with suitable amplitudes. Let's consider a signal made of the superposition of two harmonics, its mean square value is:

$$\langle x(t)^2 \rangle = \langle A^2 \sin^2(\omega_1 t + \phi) + B^2 \sin^2(\omega_2 t + \phi) + 2AB \sin(\omega_1 t + \phi) \sin(\omega_2 t + \phi) \rangle$$

$$\downarrow$$

$$= \frac{A^2}{2} + \frac{B^2}{2}$$

and it is also equal to the variance, being $\langle x(t) \rangle = 0$. Therefore the noise is equal to the sum of the variances of each harmonic contributing to the noise $x(t)$.

$$\sigma^2 = \sum_i \sigma_{fi}^2 = \int_{-\infty}^{+\infty} S(f) df$$

being $S(f)$ the POWER SPECTRAL DENSITY.

Let's consider a receiver, whose noise is due to thermal fluctuations of carriers. We may assume that the potential fluctuations have a very broad spectrum, being then made of uncorrelated signals in the time domain.


It can be considered that each component in an electronic circuit can be modelled as an equivalent PSD generator (voltage or current), whose effect is transferred to the output and is added to the other contributions to noise, being them uncorrelated.

→ RESISTORS

As already said, to first order we may assume $S(f) = W$ const (WHITE)

Let's consider this circuit
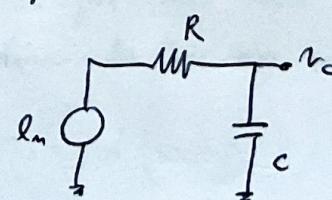
$$\frac{V_C(t)}{I_m} = \frac{1/I_C}{R + \frac{1}{I_C}} = \frac{1}{1 + R/C}$$



(5)

So

$$\begin{aligned} \langle v_c^2 \rangle &= \sigma^2 = \int_0^{+\infty} S_V(f) |T(j\omega)|^2 df = W \cdot \int_0^{+\infty} |T(j\omega)|^2 \cdot \frac{4}{\omega^2} d\omega \\ &= \frac{W}{2\pi C} \int_0^{+\infty} \frac{2\pi C df}{1 + (2\pi f)^2} = \frac{W}{2\pi C} \left[\arctan(\frac{\omega}{2\pi}) \right]_0^{+\infty} = \frac{W}{2\pi C} \cdot \frac{\pi}{2} = \frac{W}{4C} \end{aligned}$$

we call $\frac{1}{4C} = ENBW$, EQUIVALENT NOISE BANDWIDTH.

The way in the equation is

$$\frac{1}{2} C \langle v_c^2 \rangle = \left(\frac{4T}{Z} \right) \quad \boxed{\text{EQUIPARTITION PRINCIPLE}}$$

$$\langle v_c^2 \rangle = \frac{4T}{C} = \frac{W}{4RC} \Rightarrow \boxed{W = 4HTR}$$

MOSFET

• Ohmic region

$$I_{DS} = \frac{1}{2} \mu_m C_{ox} \left(\frac{W}{L} \right) \left[2(V_{GS} - V_T) (V_{DS} - V_{DS}^2) \right] \approx \mu_m C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_T) V_{DS}$$

$$R_{th} = \frac{1}{G_{th}} = \frac{1}{\mu_m C_{ox} \frac{W}{L} V_{DS}} = \frac{1}{gm} \quad \text{here a unit channel}$$

~~SHOT NOISE~~

$$S_I(Y) = \frac{4kT}{R_{th}} = 4kT gm$$

• Saturation

$$S_I(Y) = 4kT gm \quad (\text{for account for the non-uniform channel})$$

$$\left(\frac{S}{N} \right)^2 = \frac{\frac{gm \cdot V_S^2}{2}}{4kT gm \text{ BW}} = \frac{gm}{8kT \text{ BW}} \cdot V_S^2$$

By increasing gm (unit) we increase $\left(\frac{S}{N} \right)^2$, \rightarrow NOISE gets contributes on current.

REPEATED NOISE SOURCES

A theorem states that for a TWO-PORT LINEAR NETWORK (characterized by two pairs of input and output terminals), we can substitute the real network with an ideal model, one with two equivalent noise sources at the input, whose values are INDEPENDENT OF SOURCE AND LOAD IMPEDANCES.


Therefore, to compute $S_{v,eq}$ and $S_{i,eq}$, we may short the output port and take the noise of the short circuit unit as output value.

$$\begin{cases} S_{i,eq} \Rightarrow \text{open at the input} \\ S_{v,eq} \Rightarrow \text{short at the input} \end{cases}$$

→ MOSFET


It's a 2-port network, the name being a ~~common~~ common terminal for both input and output port.
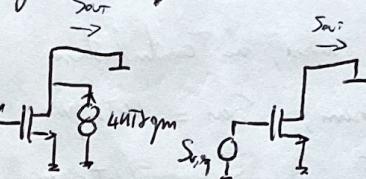
$$\begin{cases} S_{v,eq}(q) = 4kT \text{ gm} \\ S_{i,eq}(q) = S_{v,eq} \text{ gm}^2 \quad (\text{input shorted}) \end{cases}$$



$$\Downarrow \\ S_{v,eq} = \frac{4kT}{gm}$$
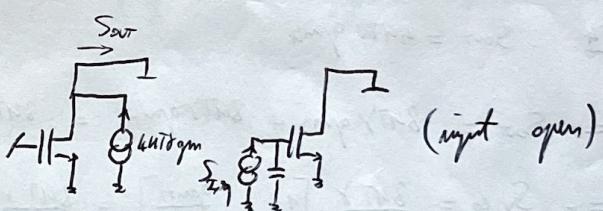
$$\begin{cases} S_{v,eq}(q) = 4kT \text{ gm} \\ S_{i,eq}(q) = S_{v,eq} \cdot \frac{gm^2}{W^2 C_L^2} = S_{v,eq} \cdot \left(\frac{W_T}{W}\right)^2 \end{cases}$$




$$\Downarrow \\ S_{v,eq} = 4kT \text{ gm } \left(\frac{W}{W_T}\right)^2$$

The relative importance of the two generators is set by the same resistance R_s

$$S_{v,inv} = S_{v,eq} + S_{i,eq} \cdot R_s^2 = \frac{4kT^2}{gm} \left[1 + (gmR_s)^2 \left(\frac{W}{W_T}\right)^2 \right]$$

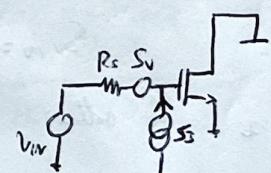as for $f \leq \frac{1}{gmR_s}$ the i_{eq} contribution is negligible.



→ DIFFERENTIAL STAGE

Strictly speaking, the differential stage is not a two-port linear network, since its output is related to signals on both input terminals. We may write

$$\begin{cases} V_1 = V_{in1} + \frac{V_d}{2} \\ V_2 = V_{in2} - \frac{V_d}{2} \end{cases}$$


$$i_{out} = (gm_2 V_1 - gm_2 V_2) = V_d \left(\frac{gm_1 + gm_2}{2} \right) + V_{in} (gm_2 - gm_1)$$

(7) If we assume $Gm_2 = Gm_1 = Gm$ then $i_{out} = Gm \cdot v_d$ and the output is proportional to the input differential voltage, so the OTA becomes a 2-port network.

DEF:

$$S_{out} = S_{v,eq} \cdot g_{m,2}^2$$
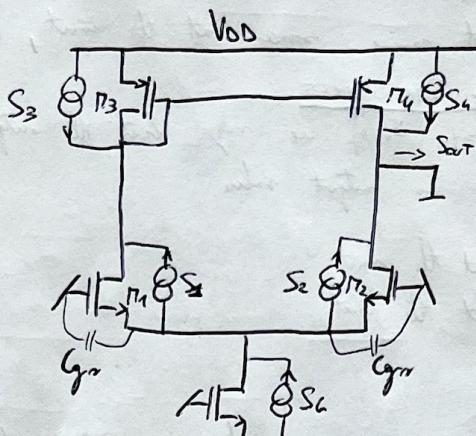
$$S_{out} = 4 S_{I,eq} \left(\frac{W_T}{W} \right)^2$$



in this case the capacitive path at the input, then it covers a feedback current in the input pair equal to $\frac{2g_m}{2L_{GS}}$, $i_{out} = \frac{2g_m}{2L_{GS}} \cdot v_d$

M_C: common mode noise, no contribution

M_I: splitting theorem, $S_{out} = 4I_{T,0} g_{m,2}$

M₂: " " , $S_{out} = 4I_{T,0} g_{m,2}$

M₃: $S_{out} = 4I_{T,0} g_{m,3}$

M₄: $S_{out} = 4I_{T,0} g_{m,4}$

$$\Rightarrow S_{out} = 8I_{T,0} g_{m,2} + 8I_{T,0} g_{m,4} = 8I_{T,0} g_{m,2} \left[1 + \frac{g_{m,4}}{g_{m,2}} \right] = \underline{S_{v,eq} g_{m,2}^2}$$

$$\Rightarrow S_{v,eq} = \frac{8I_{T,0}}{g_{m,2}} \left[1 + \frac{g_{m,4}}{g_{m,2}} \right] = \frac{8I_{T,0}}{g_{m,2}} \left[1 + \frac{V_{OD,2}}{V_{OD,4}} \right]$$

$$\Rightarrow S_{I,eq} = S_{v,eq} \cdot \frac{g_{m,2}^2}{4} \left(\frac{W}{W_T} \right)^2$$

Then this resistance again depends on the source resistance

$$S_{v,IN} = S_{v,eq} + S_{v,eq} \cdot \frac{g_{m,2}^2}{4} \cdot R_s^2 \cdot \left(\frac{W}{W_T} \right)^2$$

so the voltage noise is dominant up to $W \sim \frac{2W_T}{g_{m,2} R_s}$

→ Thermal Noise (DET.)

Let's consider two resistors R_0 connected through a lossless coaxial cable, supposed to be in thermal. The cable is said to match R_0 .

The left-hand resistor causes fluctuations that induce the resistor on the right with no reflection, being them properly matched. The noise happens on the opposite ~~direction~~ direction, and then the flows are equal because of the 2nd principle of thermodynamics. (NO NET TRANSFER OF ENERGY AT TH. EQ.)

Now, let's short the two ends, thus trapping the energy inside. This energy is distributed along the characteristic modes inside the cable, solution of the wave equations (with boundary conditions on the voltage):

$$\lambda_n = \frac{2L}{n} \quad f_n = \frac{c}{2L} \quad f_n \lambda_n = c \quad [\text{WAVE FUNCTION}]$$

so, in a frequency interval df we have

$$\frac{df}{\frac{c}{2L}} \quad (\bar{B} \text{ and } \bar{E} \text{ degrees of freedom})$$

modes, each of them having two degrees of freedom, so for the equipartition principle, kT , we

$$dE = \frac{2L}{c} kT \cdot df$$

The two energy flows are equal to \underline{P}

$$E = 2 \cdot P \cdot T = 2 \cdot \left(\frac{v_m}{2}\right)^2 \cdot \frac{1}{2R_0} \cdot \frac{L}{c}$$

$P \stackrel{\Delta}{=} \text{average power in } L$
one resistor

Considering the harmonics in the df interval, we get

$$dE = S_r \cdot df \cdot \frac{1}{2R_0} \cdot \frac{L}{c} = \frac{2L}{c} kT \cdot df$$

$$\underbrace{\left[\frac{v_m^2}{2} = \langle v_m^2 \rangle = S_r \cdot df\right]}$$

$$S_r = 4kT R_0$$

Harmonic signal

→ Junction Shot Noise


The average number of electrons crossing a junction in a μ -second is represented by the average current, while the actual number per unit time is subjected to fluctuations. It can be compared to an electron being extracted from one plate of a capacitor and reaching the other. This charge comes on a specific edge on the two plates ~~of~~ proportional to its distance from it:

9

$$\begin{cases} Q_1 = q \frac{(L-x)}{L} \\ Q_2 = q \frac{x}{L} \end{cases} \quad Q_1 + Q_2 = q$$

This induced charge carries a unit

$$\frac{dQ_2}{dt} = \left| \frac{dQ_1}{dt} \right| = \frac{q}{L} \cdot v(t) \Rightarrow \text{instantaneous carries speed}$$

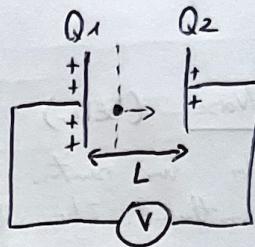

The velocity is

- ~~velocity~~ increasing proportionally to the constant electric field between the plates in the case of the charge between the capacitor's plates;
 - constant if we assume the carrier to move in a semiconductor at $v=v_{sat}$;
- in both cases, we get $\int_0^T i(t) dt = q$, being it a discrete pulse of a constant duration T .

We can divide the current in a situation as the superposition of many discrete current pulses starting at random time instants, namely

$$q h(t) \quad [h(t) \stackrel{\text{def}}{=} \text{normalized shape of the pulse}]$$

We call

$$\lambda = \frac{I}{q} \quad [\text{average number of carriers crossing the }]$$

[situation per-unit time]

Let's consider a current measured at $t = \bar{t}$, we can say that it is given by the superposition of all the pulses started at $t < \bar{t}$, so

$$i(t) = q h(t_1) + q h(t_2) + \dots$$

To switch from discrete to continuous we must weight every contribution for the probability for a pulse to occur between t_1 and $t_1 + dt$, so λdt

$$\langle i(t) \rangle = \int_0^{+\infty} h(t) q \lambda dt = q \lambda = I \quad \checkmark$$

Similarly we can compute the average square value: Squared Values Cross Products

$$\langle i^2(t) \rangle = [q h(t_1) + q h(t_2) + \dots]^2 = q^2 h^2(t_1) + q^2 h^2(t_2) + \dots + q h(t_1) q h(t_2) + \dots$$

$$\downarrow \quad \int_0^{+\infty} \int_0^{+\infty} \langle i^2(t) \rangle dt = \int_0^{+\infty} \int_0^{+\infty} (q^2 h^2(t) dt + q h(t) q h(t') dt' dt) = q^2 \lambda \int_0^{+\infty} h^2(t) dt + (q \lambda)^2$$

using that the variance of an cosed variable is

$$\sigma_x^2 = \langle x^2 \rangle - \langle x \rangle^2$$

we may write

$$\begin{aligned}\sigma_x^2 &= \langle i^2 \rangle - \langle i \rangle^2 = \int_0^{+\infty} h^2(t) dt (q^2)\lambda + (q\lambda)^2 - (q\lambda)^2 = q^2 \lambda \int_0^{+\infty} h^2(t) dt \\ &\downarrow \\ &= q I \int_0^{+\infty} h^2(t) dt\end{aligned}$$

Now, using the Parseval theorem, we can write

$$\int_0^{+\infty} |h(t)|^2 dt = \int_{-\infty}^{+\infty} |h(\gamma)|^2 d\gamma = 2 \int_0^{+\infty} |H(\gamma)|^2 d\gamma$$

$h(t)$ real $\Leftrightarrow |H(\gamma)|$ even function

So, in the end, we get

$$\sigma_x^2 = 2q I \int_0^{+\infty} |H(\gamma)|^2 d\gamma = \int_0^{+\infty} S_I(\gamma) d\gamma = 2q^2 \lambda \int_0^{+\infty} |H(\gamma)|^2 d\gamma$$

and from the equation we derive

$$S_I(\gamma) = 2q I |H(\gamma)|^2$$

Finally, since our pulses have a duration T of the order of μs , then the amplitudes of this Fourier transform will be $\approx 100 \text{ MHz}$, so to fit with we can consider $|H(\gamma)|^2 \approx 1$ in the BW of interest.

Accounting for both physical mechanism involved in diode's circuit (DRIFT + DIFFUSION) we get that

$$S_I = 2q (I + 2I_0) \quad \begin{cases} I_{DRIFT} = I + I_0 \\ I_{DIFFUSION} = -I_0 \end{cases}$$

So, we get

$$\underline{\text{REVERSE BIAS}} \Rightarrow S_I = 2q I_0$$

$$\underline{\text{FORWARD BIAS}} \Rightarrow S_I \approx 2q I$$

$$\underline{\text{ZERO BIAS}} \Rightarrow S_I = 4q I_0 = 4q kT \frac{I_0}{hT} = 4kT g_{m,0}$$

(11) Finally, we can say that also the count in near-intrinsic PNPETS is affected by shot noise, being it caused by the superposition of count pulses generated by ionizing particles above the barrier.

$$S_I = 2g \cdot I_D = 2g \cdot I_D \cdot \frac{mV_{DD}}{mV_{TH}} = 2g \cdot \frac{4kT}{q} \cdot gpm = 4kT \frac{g}{2} gpm = 4kTg gpm$$

where $\gamma = \frac{g}{2}$

→ RTN

Let's consider a unit made of n-Si. The average count flux through it is

$$I = \frac{V}{R} = V \frac{W \cdot \Delta}{L} gpm = gpm \cdot \frac{N}{L^2} V \quad (I \propto N)$$

being N the total number of free carriers in a volume $V = W \cdot \Delta \cdot L$

If a carrier is trapped or emitted by a trap, this causes a reduction or an increase of the total count. Each count covers a portion of N equal to ΔN , and so

$$\frac{\Delta I}{I} = \frac{\Delta N}{N} \Rightarrow \Delta I = \frac{I}{N} \quad (\text{for } \Delta N=1)$$

Each trapping or emission event covers count variations that happen to nearly the steady state value exponentially, and the time needed to occur it is a statistical variable. So we can write each pulse here:

$$i(t) = \Delta I \cdot e^{-\frac{t}{\tau}} = (\Delta I \cdot \bar{e}) \cdot \frac{1}{\bar{e}} e^{-\frac{t}{\bar{e}}} = Q \cdot \bar{e} i(t)$$

At steady state λ (# of emission events per unit time) is equal to # of capture events per unit time. We expect

$\lambda \propto N_T$ (number of traps in the volume)

$$\downarrow \\ \lambda = \beta \frac{N_T}{\bar{e}}$$

As already shown for the p-n junction, a noise characterized by the superposition of well-defined count pulses of area Q can be written as

$$\begin{aligned} S_I(Q) &= 2\lambda Q^2 |H(Q)|^2 = 2\lambda Q^2 \frac{1}{(1+w^2\bar{e}^2)} \\ &\downarrow \\ &= 2\beta \frac{N_T}{\bar{e}} \Delta I^2 \cdot \bar{e}^2 \cdot \frac{1}{1+w^2\bar{e}^2} = 2\beta N_T \Delta I^2 \frac{\bar{e}}{1+w^2\bar{e}^2} \\ &\downarrow \\ &= 2\beta N_T \left(\frac{I}{N}\right)^2 \frac{\bar{e}}{1+w^2\bar{e}^2} \end{aligned}$$

This contribution is equal to the one due to emission events, being them statistically independent from the capture events.

so we get

$$S_I(Y) = 4\beta N_T \left(\frac{I}{N}\right)^2 = \frac{c}{(1+w^2 z^2)}$$

Lorentzian
shape

value

$$\beta = \frac{2e^2 c}{(2e + 2c)^2} \quad z = \frac{2e^2 c}{2e + 2c}$$

symmetry coeff. const,
maximum for $2e = 2c$
and equal to $\frac{1}{4}$
given by others at the Fermi level

$$S_I(Y) = N_T \cdot \left(\frac{I}{N}\right)^2 \frac{c}{1+w^2 z^2}$$

→ $1/f$ Noise

Defects with different true currents may exist, so let's introduce the function $g(z)$ which is a ~~uniform~~ distribution of defects over the z axis, so that

$$dN_T(z) = N_T g(z) dz \quad (g(z) \text{ is normalized})$$

therefore we can write

$$S_I(Y) = N_T \cdot \left(\frac{I}{N}\right)^2 \int_{z_{min}}^{z_{max}} \frac{g(z) z}{1+w^2 z^2} dz$$

$\left\{ z_{min} = \text{width } z \text{ that can be measured, not by the BW of the operators} \right.$
 $\left. z_{max} = \text{not by the apparent duration} \right.$

M. Whelan pointed out that in a MOSFET few carriers can be captured by defects at the interface and move it, due to tunneling. Defects in the oxide have $z = z_0 e^{rx}$ $\left\{ z_0 \text{ height of the barrier} \right.$
 $\left. z_0 \pm \sigma \text{ for defects at the interface} \right.$

Let's consider defects to be distributed uniformly all over the oxide thickness

$$n_r = \frac{N_T}{t_{ox}} \quad [\text{density per unit length}]$$

so we can write

$$n_r dx = N_T \frac{dz}{t_{ox}} = N_T g(z) dz$$

and

$$dz = z_0 e^{rx} dx = z dx \Rightarrow dx = \frac{dz}{z_0 e^{rx}}$$

so

$$g(z) = \frac{1}{z_0 t_{ox}} \quad (\text{we've limited } g(z) \text{ to other points we need})$$

(13)

$$\Rightarrow S_I(Q) = \frac{N_T}{\gamma \tau_{ox}} \left(\frac{I}{N}\right)^2 \int_{w_{min}}^{w_{max}} \frac{dw}{1 + w^2 c^2} = \frac{N_T}{\gamma \tau_{ox}} \frac{1}{w} \left(\frac{I}{N}\right)^2 \left[\arctan(wc) \right]_{w_{min}}^{w_{max}}$$

$$= \frac{N_T}{\gamma \tau_{ox}} \frac{1}{w} \left(\frac{I}{N}\right)^2 [\arctan(wc_{max}) - \arctan(wc_{min})]$$

Considering $wc_{max} \gg 1$ and $wc_{min} \ll 1$ we get

$$S_I(Q) = \frac{N_T}{\gamma \tau_{ox} w} \left(\frac{I}{N}\right)^2 \frac{\pi}{2} = \frac{N_T}{4 \gamma \tau_{ox}} \left(\frac{I}{N}\right)^2 \cdot \frac{1}{f}$$

Transistor Formula

$$N = C_{ox} (WL) (V_L - V_T) \cdot \frac{1}{q} \quad \text{carries in the channel}$$

$$N_T = M_T \cdot WL \tau_{ox} \quad \frac{\text{charges}}{\text{in the oxide}}$$

$$S_I(Q) = \frac{M_T \cdot WL \cdot \tau_{ox}}{4 \gamma \tau_{ox} \cdot 4} q^2 \frac{\left[\frac{1}{2} M_T C_{ox} \left(\frac{W}{L} \right) (V_L - V_T)^2 \right]^2}{\left[C_{ox} (WL) (V_L - V_T) \right]^2} \cdot \frac{1}{f}$$

$$= \frac{M_T \cdot WL \cdot q^2}{4 \cdot \gamma (WL)^2} \cdot \frac{1}{f} \cdot \frac{1}{4} \mu_m^2 \cdot \left(\frac{W}{L} \right)^2 \cdot (V_L - V_T)^2 -$$

$$= \frac{M_T q^2}{8 \gamma L^2} \cdot \frac{\mu_m}{C_{ox}} \cdot \frac{I}{f} = \frac{K_T^{1/4}}{L^2} \cdot \frac{I}{f}$$

$$S_V(Q) = qm^{-2} S_I(Q) = \frac{M_T \mu_m q^2}{8 \gamma C_{ox} L^2} \cdot \frac{1}{f} \cdot \frac{V_{ov}^2}{4 \cdot I^2} = \frac{1}{f} \frac{M_T}{16 \gamma C_{ox}} \cdot \frac{1}{2} \mu_m C_{ox} \left(\frac{W}{L} \right) V_{ov}^2 \cdot \frac{1}{f} \cdot \frac{1}{C_{ox} WL}$$

$$= \frac{1}{f} \frac{M_T q^2}{16 \gamma C_{ox}} \cdot \frac{1}{C_{ox} WL} = \frac{K_V^{1/4}}{C_{ox} WL} \cdot \frac{1}{f} \checkmark$$

PROTOTYPICAL DIFFERENTIAL STAGE

(14)

Differential amplifier \Rightarrow amplifies the potential difference, regardless of the average potential


$$CMRR \triangleq \left| \frac{G_d}{G_{av}} \right|$$

① RESISTANCES

$$G_d = \frac{g_m R_L}{2} = \frac{I R_L}{V_{DD}}$$

$$G_{av} = \frac{-v_{av}}{2R_E + \frac{1}{g_m}} \cdot R_L \approx -2g_m \frac{R_L}{2R_E} \quad (\text{HALF CIRCUIT})$$
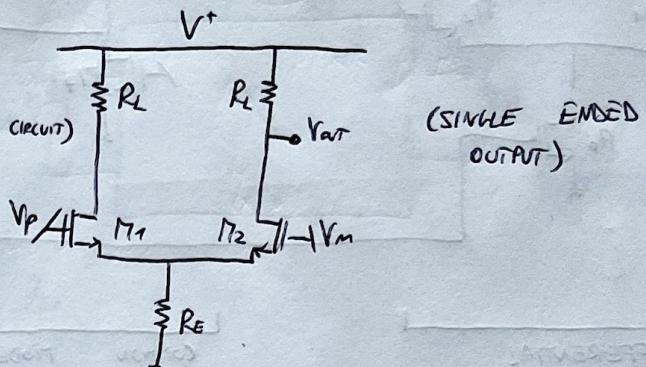
$$CMRR = \frac{g_m R_L}{2} \cdot \frac{2R_E}{R_L} = g_m R_E$$



$G_{d,max}$ limited by $I \cdot R_L = V_{L,max}$ (M_1 & M_2 may become linear)

$CMRR_{max}$ limited by the maximum current I , which is limited by the maximum V_{DD} .

② CURRENT GENERATORS

We may think to improve R_{av} without having to deal with high voltage drops by replacing R_E with current generators.


Similarly, we should also replace R_L by substituting it with a current generator.

$$G_{av} = \frac{r_o}{2R_E}$$

$$G_d = \frac{g_m r_o}{2}$$

$$CMRR = \frac{g_m r_o}{2} \cdot \frac{2R_E}{r_o} = g_m R_E$$


Maybe improve $r_{o,g}$ using CASCODES!

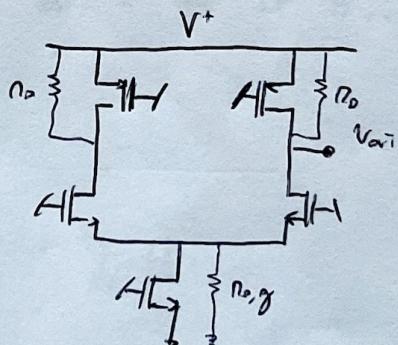

③ COMMON MODE FEEDBACK

The previous circuit indeed needs to have the two transistors perfectly matching the MOS current, otherwise the intermediate drain nodes will be out of balance to push the upper or lower pair into the linear region, until the units match. Other transistors though have lower $r_{o,g}$ so larger $G_d \Rightarrow \text{BAD!}$

We need feedback:

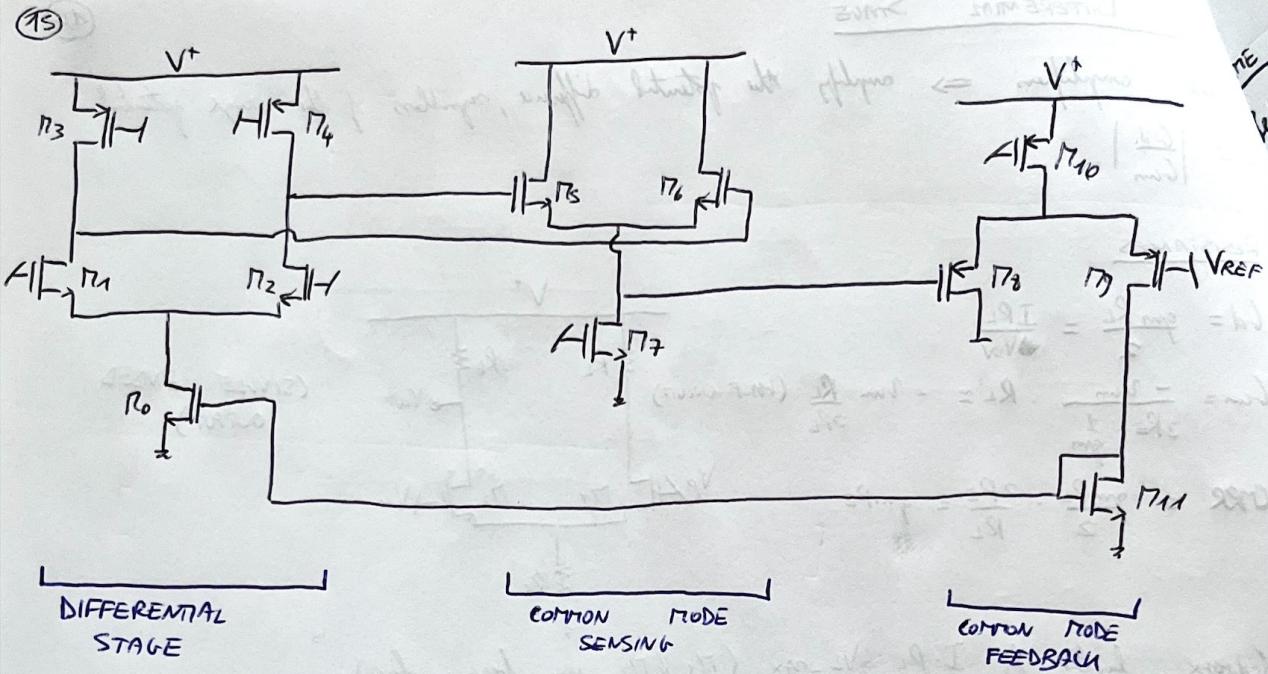

TIME CONSTANTS METHOD


Let's consider a linear time-invariant network with a resistor R_m and one capacitor:

Input Variables: i_C & V_{IN}

Output Variables: V_{OUT} & V_C


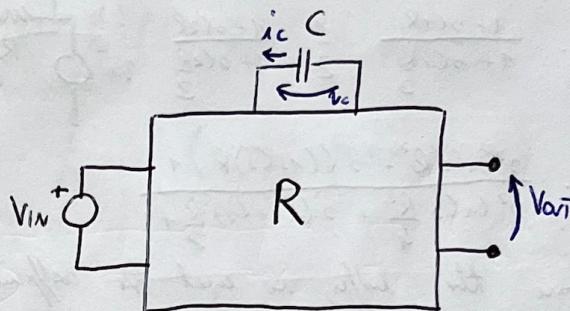
$$\left\{ \begin{array}{l} V_{OUT} = A_0 V_{IN} + R_m i_C \\ V_C = B_0 V_{IN} + R_1 \cdot i_C \end{array} \right.$$



$(A_0, B_0, R_m, R_1) \in \mathbb{R}$ being the core resistive.

Let's consider that $V_C = -\frac{i_C}{RC}$



$$\left\{ \begin{array}{l} V_{OUT} = A_0 V_{IN} - \sigma C R_m i_C \\ V_C = B_0 V_{IN} - \sigma C R_1 i_C \end{array} \right. \Rightarrow i_C = \frac{B_0 V_{IN}}{1 + \sigma C R_1}; \quad V_{OUT} = A_0 V_{IN} \left[1 - \sigma C \frac{R_m B_0 / A_0}{1 + \sigma C R_1} \right]$$

$$V_{OUT} = A_0 V_{IN} \frac{1 + \sigma C (R_1 - R_m B_0 / A_0)}{1 + \sigma C R_1}$$

So we have a pole at $\sigma = -\frac{1}{CR_1}$ and a zero at $\sigma = -\frac{1}{C(R_1 - R_m B_0 / A_0)}$
For a zero to exist it must be

$$A_0 V_{IN} + R_m i_C = 0$$



$$i_C = -\frac{A_0}{R_m} V_{IN} \quad \text{or} \quad V_{IN} = -\frac{R_m}{A_0} i_C$$

So

~~REZISTOR SEEN ACROSS C WHEN $V_{OUT} = 0$~~

$$V_C = -\frac{B_0}{A_0} R_m i_C + R_1 i_C$$



$$\frac{V_C}{i_C} = \left(R_1 - \frac{R_m B_0}{A_0} \right) = R_{eq}$$


[RESISTANCE SEEN ACROSS C WHEN $V_{OUT} = 0$]

$$\Rightarrow \frac{V_{OUT}}{V_{IN}} = A_0 \frac{1 + \sigma C R_{eq}}{1 + \sigma C R_1}$$

17 Let's consider now two RC networks decoupled by a buffer, the overall T.F. will be the cascade of the two:

$$T(s) = \frac{1}{2} \cdot \frac{1 + sC_1R}{1 + sC_1\frac{R}{2}} \cdot \frac{1}{2} \cdot \frac{1 + sC_2R}{1 + sC_2\frac{R}{2}}$$
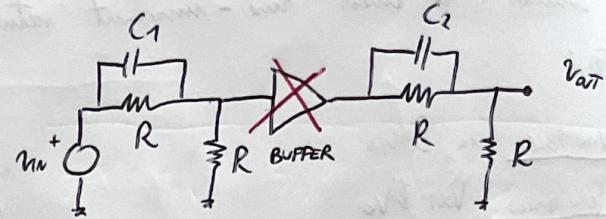
$$= \frac{1}{4} \cdot \frac{s^2 C_1 C_2 R^2 + 2(C_1 + C_2)R + 1}{s^2 C_1 C_2 \frac{R^2}{4} + 2(C_1 + C_2)\frac{R}{2} + 1}$$



If we remove the buffer, we expect the coefficients to change, but just for the resistive part. Moreover, also the DC gain changes!

$[A_0 \stackrel{\text{DEF}}{=} \text{GAIN WITH ALL THE CAPACITORS OPEN}]$

① $C_2 \rightarrow 0$

$$T(s) = A_0 \frac{s(C_1 d_1 + 1)}{s(C_1 \beta_1 + 1)}$$

and we know that $d_1 = R_{1,0}^{(0)}$ $\beta_1 = R_1^{(0)}$

~~$$T(s) = A_0 \frac{s^2(C_1 d_1 d_2 + s(C_1 d_1 + C_2 d_2) + 1)}{s^2(C_1 d_2 \beta_1 + s(C_1 \beta_1 + C_2 \beta_2) + 1)}$$~~

② $C_1 \rightarrow 0$

$$T(s) = A_0 \frac{s(C_2 d_2 + 1)}{s(C_2 \beta_2 + 1)}$$

and we know that $d_2 = R_{2,0}^{(0)}$ $\beta_2 = R_2^{(0)}$

③ $C_1 \rightarrow \infty$ (a short)

$$T(s) = A_0 \frac{s^2(C_1 C_2 d_{12} + s(C_1 R_{01}^{(0)})}{s^2(C_1 C_2 \beta_{12} + s(C_1 R_1^{(0)}))} = A_0 \frac{s^2 C_1 C_2 d_{12} + C_1 R_{01}^{(0)}}{s^2 C_1 C_2 \beta_{12} + C_1 R_1^{(0)}} =$$

$$= A_0 \frac{R_{01}^{(0)}}{R_1^{(0)}} \frac{s C_2 d_{12} / R_{01}^{(0)} + 1}{s C_2 \beta_{12} / R_1^{(0)} + 1}$$

and since the network can be seen as the one of a single capacitor C_2 and C_1 as a short, we may write

$$\begin{cases} \frac{d_{12}}{R_{01}^{(0)}} = R_{02}^{(1)} \\ \frac{\beta_{12}}{R_1^{(0)}} = R_2^{(1)} \end{cases} \Rightarrow \begin{cases} d_{12} = R_{01}^{(0)} R_{02}^{(1)} \\ \beta_{12} = R_1^{(0)} R_2^{(1)} \end{cases}$$

If we chose $C_2 \rightarrow \infty$ instead of C_1 , we'd get

$$\begin{cases} d_{12} = R_{02}^{(0)} R_{01}^{(1)} \\ \beta_{12} = R_2^{(0)} R_1^{(2)} \end{cases}$$

which must be equal to the one obtained for $C_1 \rightarrow \infty$, otherwise the T.F. is wrong!

→ POLAROID RESULTS

Starting from a 3rd order T.F., we may write

$$D(s) = b_3 s^3 + b_2 s^2 + b_1 s + 1 = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right)$$

$$b_1 = - \left(\frac{1}{p_1} + \frac{1}{p_2} + \frac{1}{p_3} \right) \approx - \frac{1}{p_1} \quad (\text{assuming } p_1 \ll p_2, p_3)$$


Q MF

$$D(s) \approx b_3 s^3 + b_2 s^2 = s^2(b_3 s + b_2) = 0$$

$$p_3 \approx - \frac{b_2}{b_3} = \text{residue thus...}$$

→ MILLER THEOREM

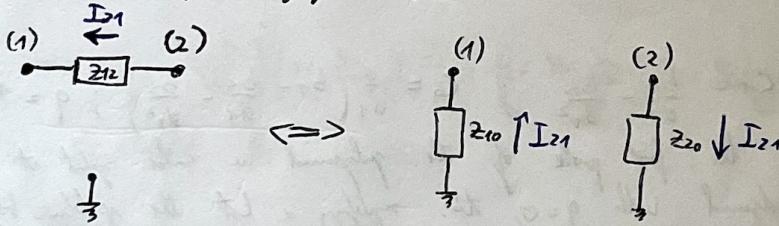We want to replace Z_{12} with two resistors Z_{10} and Z_{20} , we must set that the input entering or going out of the nodes remain unchanged



$$I_{21} = \frac{V_2 - V_1}{Z_{12}} = -\frac{V_1}{Z_{10}} \quad \left[\frac{V_2}{V_1} = K(\gamma) \right]$$



$$V_2 - V_1 = -\frac{Z_{12}}{Z_{10}} V_1$$



$$Z_{10} = -\frac{V_1}{V_2 - V_1} \cdot Z_{12} = \frac{V_1}{V_1 - V_2} Z_{12}$$



$$\Rightarrow Y_{10} = \frac{V_1 - V_2}{V_1} Y_{12} = [1 - K(\gamma)] Y_{12}$$

$$I_{21} = \frac{V_2 - V_1}{Z_{12}} = \frac{V_2}{Z_{20}}$$



$$Z_{20} = \frac{V_2}{V_2 - V_1} Z_{12}$$



$$Y_{20} = \frac{V_2 - V_1}{V_2} Y_{12}$$

$$\Rightarrow Y_{20} = \frac{K(\gamma)}{1 - K(\gamma)} Y_{12}$$

→ APPROXIMATIONS AND CIRCUIT INSIGHTS

It's important to derive some estimates of the poles and zeros by using approximations in order to understand which parameters are limiting the stability. Let's consider a third order T.F. for example:

$$D(s) = b_3 s^3 + b_2 s^2 + b_1 s + 1$$

(19) We may divide it for first order terms

$$(b_3 z^3 + b_2 z^2 + b_1 z + 1) \div (d_1 z + 1)$$

$$\begin{aligned} & \overline{b_3 z^3 + b_2 z^2 + b_1 z + 1} \\ & \overline{b_3 z^3 + \frac{b_3}{d_1} z^2} \\ & \approx \left(b_2 - \frac{b_3}{d_1} \right) z^2 + b_1 z + 1 \\ & \overline{\left(b_2 - \frac{b_3}{d_1} \right) z^2 + \frac{1}{d_1} \left(b_2 - \frac{b_3}{d_1} \right) z} \\ & \approx \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) z + 1 \\ & \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) z + \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) \end{aligned}$$

$$\frac{d_1 z + 1}{\begin{aligned} & b_3 z^2 + \frac{1}{d_1} \left(b_2 - \frac{b_3}{d_1} \right) z + \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right) \end{aligned}}$$

So we get

$$c_2 z^2 + c_1 z + q + \frac{1}{d_1 z + 1}$$

where

$$c_2 = \frac{b_3}{d_1}; \quad c_1 = \frac{b_2}{d_1} - \frac{b_3}{d_1^2}; \quad q = \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right); \quad q = 1 - \frac{1}{d_1} \left(b_1 - \frac{b_2}{d_1} - \frac{b_3}{d_1^2} \right)$$

If $-\frac{1}{d_1}$ was exactly the first pole of the polynomial we could split it into a 2nd and a 1st order polynomial with $q=0$, this simplifying a lot the problem. However, even if we don't have exactly p_1 , we have that it is = not by the Miller's approximation, so we may say

$$p_1 \approx -\frac{1}{b_1}$$

so we get

$$c_2 = \frac{b_3}{b_1}; \quad c_1 = \frac{b_2}{b_1} - \frac{b_3}{b_1^2}; \quad q = \frac{1}{b_1} \left[b_1 - \frac{b_2}{b_1} - \frac{b_3}{b_1^2} \right]; \quad q = \frac{1}{b_1} \left(b_2 - \frac{b_3}{b_1^2} \right)$$

and split the denonator like this

$$(c_2 z^2 + c_1 z + 1)(1 + z b_1)$$

only $q \approx 0$. It can be shown that these results are really close to the ones obtained by shorting CC and cutting the running poles using the extended trapezoidal method.

The single-ended configuration is another option to guarantee consistent bias of the stage. The adoption of the current mirror leaves the current from I_{L1} to the current delivered by the tail, hence injecting the control logic directly in the differential stage.

In order for the bias to be consistent, we need

$$\begin{cases} I_1 = \bar{I}_3 \\ I_2 = \bar{I}_4 \end{cases}$$

(neglecting V_{AV} in $(V_{AS} - V_{AV})/V_A$)

$$\frac{1}{2} \mu_m C_{\text{ox}} \left(\frac{V_A}{L} \right)_1 \left(V_{\text{ox},0} \right)^2 \left[1 + \frac{V_K - V_S}{V_A} \right] = I_1$$

$$\frac{1}{2} M_P C_{\alpha x} \left(\frac{\psi}{L} \right)_3^2 \left(\text{Var}_{\beta y} \right)^2 \left[1 + \frac{V_{DD} - V_X}{V_A} \right] = I_3$$

$$\frac{1}{2} \mu_m C_{\text{ox}} \left(\frac{W}{L} \right)_2 \left(V_{\text{out},2} \right)^2 \left[1 + \frac{V_{\text{out},2} - V_A}{V_A} \right] = I_2$$

$$\frac{1}{2} M_p C_0 \times \left(\frac{W}{L}\right)_4 (V_{out,n})^2 \left[1 + \frac{V_{DD} - V_{out}}{V_A} \right] = I_4$$

$$\frac{I_1}{I_2} = \frac{I_3}{I_4} \Rightarrow \left(1 + \frac{V_{X3} - V_S}{V_A}\right) \left(1 + \frac{V_{DD} - V_{out}}{V_A}\right) = \left(1 + \frac{V_{DD} - V_X}{V_A}\right) \left(1 + \frac{V_{out} - V_S}{V_A}\right)$$

by injection it turns out that $Vx = V_{\alpha\beta}$

\rightarrow VOLTAGE SWINGS

$$-V_{CM,max} = V_{DD} - V_{S3,3} + |V_T| = V_{DD} - V_{A,3} - |V_H| + |V_T| = V_{DD} - V_{A,3} \quad (\text{Saturation of } M_1)$$

$$\bullet \text{Var}_{17/N} = \text{Var}_{\alpha_0} + \text{Var}_{\beta_1} = \text{Var}_{\alpha_0} + \text{Var}_{\beta_1} + \text{Var}_{\epsilon} \quad (\text{Saturation of Mo})$$

Not symmetric! Towards ground it has to accommodate for a V_{ds} in addition to an overdrive voltage.

$$\text{Var}_{\text{MIN}} = \text{Var}_{\text{MIN}} - |\text{Var}| = \text{Var}_{\text{o}} + \text{Var}_{\text{r}} \quad (\text{Saturation of } \text{I}_2)$$

$$\text{• } V_{\text{out}} |_{M_4} = V_{DD} - V_{DSS_4} \quad (\text{Saturation of } M_4)$$

→ DIFFERENTIAL GAIN

Due to the introduction of the mirror, the circuit is not symmetric anymore, since the resistances on the chain of T_1 and T_2 are different! In order to restore symmetry, we use the Norton theorem:

- in order to compute ice we need to short the sum of M_4 . In this way both the sum of M_1 and M_2 are connected to law-2 values, we can assume them to be zero with an error of $\frac{1}{gm^2}$.

(21) Now we've restored symmetry and we see that midiff splits evenly on the two transistors, thus being the same state on small signal operation. Neglecting also the mirroring error, we get

$$i_{CC} = g_{m1} \text{midiff}$$

- R_{out} can be computed by noticing that we have a loop acting to fix V_{out} to V_{DD} , so we may cut the loop, recompute the midpoint (V_{mid}) and compute



$$\text{loop}(0) = -1$$

$$R_{out}^{(0)} = 2R_{D2}$$

$$R_{out} = R_{out}^{(0)} \parallel R_{D4} = \frac{R_{out}^{(0)}}{1 - \text{loop}(0)} \parallel R_{D4} = R_{D2}/R_{D4}$$

In the end we get
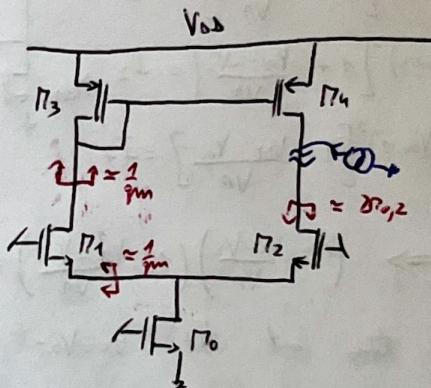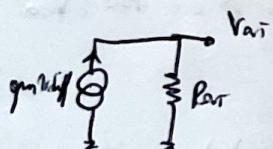
$$G_{D1} = g_{m1} \cdot R_{out} = \frac{k}{2}$$




COMPENSATION (Two-STAGE)

MILLER

Split the two poles due to the two high impedance nodes by placing a C_1 bridging the gate-drain nodes of a transistor.

The three capacitors are dependent (they form a loop) so we expect only two poles in the T.F.:
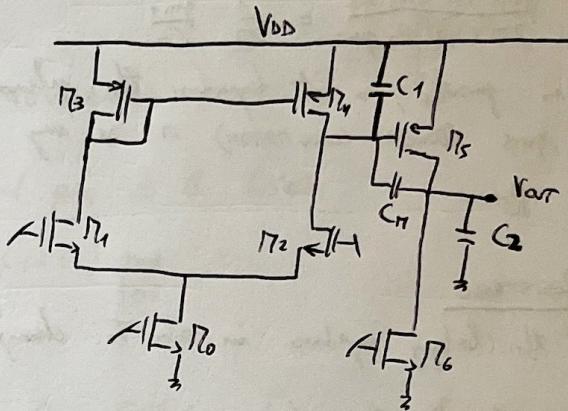
$$b_1 = C_1 \cdot R_1^0 + C_2 R_2^0 + G_1 R_1^0$$



$$\left\{ \begin{array}{l} R_1^0 = R_{out,1} = R_1 \\ R_2^0 = R_{out,2} = R_2 \end{array} \right.$$

$$\left\{ \begin{array}{l} R_{in}^0 = R_1 + g_{ms} R_2 R_1 + R_2 \quad (\text{Miller effect}) \\ b_1 = C_1 R_{out,1} + R_2 (C_L + C_1) + (1 + g_{ms} R_2) C_1 R_1 = \tilde{\epsilon}_1 + \tilde{\epsilon}_2 + \tilde{\epsilon}_3 \end{array} \right.$$

$$\Rightarrow b_1 = C_1 R_{out,1} + R_2 (C_L + C_1) + (1 + g_{ms} R_2) C_1 R_1 = \tilde{\epsilon}_1 + \tilde{\epsilon}_2 + \tilde{\epsilon}_3$$

$$b_2 = C_1 G_1 R_1^0 R_2^0 + C_1 G_1 R_1^0 R_{in}^0 + G_2 G_1 R_2^0 R_{in}^0$$

$$\left\{ \begin{array}{l} R_1^0 = R_2 \\ \cancel{R_{in}^0} = R_2 \\ R_{in}^2 = R_1 \end{array} \right.$$

$$\Rightarrow b_2 = G_1 R_2 (C_2 + G_1) + R_1 R_2 C_2 G_1 = \tilde{\epsilon}_1 \tilde{\epsilon}_2 + \tilde{\epsilon}_4$$

$$b_3 = C_1 C_2 G_1 R_1^0 R_2^0 R_{in}^{1,2} = 0 \quad (\text{as expected})$$

We expect also a zero when

$$2C_{in}V_{ds} = g_{ms}V_S$$

$$2 = \frac{g_{ms}}{C_{in}} \quad (\text{POSITIVE})$$

If the roots of the denominator are split of more than a decade, we get

$$P_L \approx -\frac{1}{b_1} \approx -\frac{1}{R_1 g_{ms} R_2 G_1}$$

$$P_H \approx -\frac{b_1}{b_2} \approx -\frac{R_1 g_{ms} R_2 G_1}{R_1 R_2 C_1 (C_2 + G_1) + R_1 R_2 C_2 G_1} = -\frac{g_{ms} C_1}{C_1 C_2 + C_1 G_1 + C_2 G_1}$$

(23)

For large C_1 values we get


$$P_H \approx -\frac{g_{ms}}{C_1 + C_2}$$

and P_L moves to lower frequencies.

Finally, we have

$$\text{LBWDP} = \frac{g_{ms} R_1 g_{ms} R_2}{2\pi (C_1 P_L R_2 g_{ms})} = \frac{1}{2\pi} \frac{g_{ms}}{C_1}$$

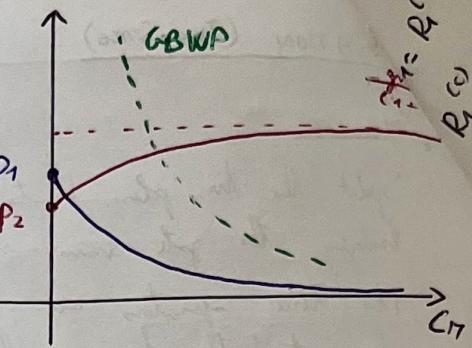The zero is positive, so it degrades the phase margin! We must shift it to HF by increasing g_{ms} (POWER CONSUMPTION) or we may increase C_1 in order to move P_L away from P_H .



NULLING RESISTANCE

We modify the bulging impedance in order to change the zero:

$$\frac{V_S}{R_N + \frac{1}{g_{ms} C_1}} = g_{ms} Z_S$$

↓

$$Z_S = -\frac{1}{C_1 \left[R_N + \frac{1}{g_{ms}} \right]}$$

We may now R_N in order to have a negative zero canceling out with the second pole.

Owing to R_N we have three poles

$$b_1 = C_1 R_1 + \cancel{C_2 R_2} + C_c (R_1 + R_2 + g_{ms} R_1 R_2 + R_N)$$

being $R_N \approx \frac{1}{g_{ms}}$ we repeat

$$b_1 \approx C_1 g_{ms} R_1 R_2 \quad (\text{UNCHANGED})$$

$$\Rightarrow Z_L \approx b_1 ; P_L = -\frac{1}{b_1}$$


We can compute Z_M using the time constant method:

$$\left\{ \begin{array}{l} Z_1^\infty = (R_1/R_N) C_1 \approx R_N C_1 \\ Z_2^\infty = (R_2/R_N) C_2 \approx R_N C_2 \end{array} \right.$$

$$Z_C^\infty = R_N$$

$$P_H = -\left(\frac{1}{Z_1^\infty} + \frac{1}{Z_2^\infty} + \frac{1}{Z_C^\infty}\right) \approx -\frac{1}{R_N (C_1/C_2/C_C)}$$

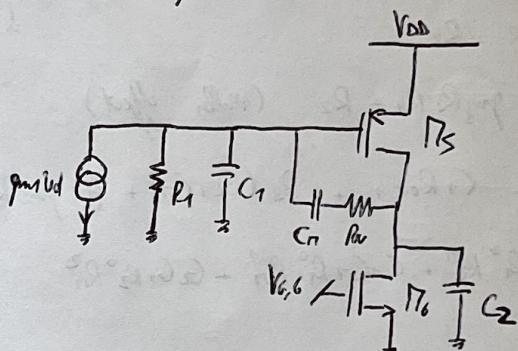We can compute the real pole assuming that C_C is a short (this approximation is clearly justified in "APPROXIMATIONS AND CIRCUIT INSIGHTS")



in series to the resistance across gate and drain of M_S

$$b_1 = R_1^{(c)} c_1 + R_2^{(c)} c_2$$

$$R_1^{(c)} = R_{11} \left[\frac{R_1 + R_2}{1 + g_{MS} R_2} \right] \approx \frac{1}{g_{MS}}$$

$$R_2^{(c)} = R_2 // \left[\frac{R_N + R_L}{1 + g_{MS} R_L} \right] \approx \frac{1}{g_{MS}}$$

$$P_2 \approx - \frac{1}{(C_1 + C_2) \frac{1}{\text{rms}}} = - \frac{\text{rms}}{(C_1 + C_2)} \quad (\text{UNCHANGED})$$

Therefore if we place the second pole at the CBWP:

$$\frac{C_1}{q_{MS}} = \frac{C_1 + C_2}{q_{MS}} \Rightarrow C_M = (C_1 + C_2) \frac{q_{MS}}{q_{MS}}$$

~~them~~

$$\left[\text{Re} - \frac{1}{g_{\text{ms}}} \right] S_{\text{Tr}} = \frac{S_{\text{Tr}}}{g_{\text{ms}}} \Rightarrow \text{Re} = \frac{S_{\text{Tr}}}{g_{\text{ms}}} \left(\frac{1}{g_{\text{ms}}} + \frac{1}{g_{\text{ms}}} \right) = \frac{2}{g_{\text{ms}}} \quad (\text{if } g_{\text{ms}} = g_{\text{ms}})$$

We may implement the resistor by using a MOSFET in one region

$$I_{DS} = \frac{1}{2} \mu_m C_{ox} \sum [(V_{GS} - V_T) V_{DS,2} - V_{DS}^2]$$

$$g_0 = \left. \frac{\partial I(DS)}{\partial V(DS)} \right|_{V(DS)=0} = \frac{1}{2} \mu_m C_{DS} \frac{W}{L} (2V_{DS})$$

therefore we need

$$\frac{g_{ms}}{g_0} = 2 \Rightarrow \frac{(W/L)_S}{(W/L)_R} \frac{Var_S}{Var_R} = 2$$


If we set carefully $\text{Var}_S = \text{Var}_R$, then the accuracy depends on a ratio, which is optimal in integrated design. In order to achieve this result we need to REPLICATE the bias conditions of P_S :

I_{L5} and I_{L6} are used in order to carry the same current with $V_{ad} = \frac{V_{dd}}{2}$. This current is set by the reference branch of I_{L7} , which can be set to be $\frac{1}{7}$ of I_G by setting the


$$\text{choose } \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_0 = \left(\frac{W}{L}\right)_3, \text{ then}$$

$$|\nabla_{\mathcal{S},8}| = |\nabla_{\mathcal{S},9}| = |\nabla_{\mathcal{S},5}|$$

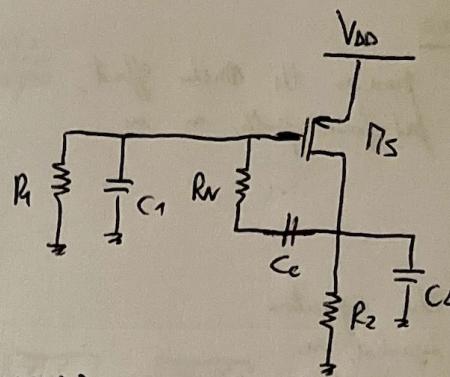Therefore the portion of the ex-exports only on the ratio of $\frac{(W/L)_S}{(W/L)_R}$



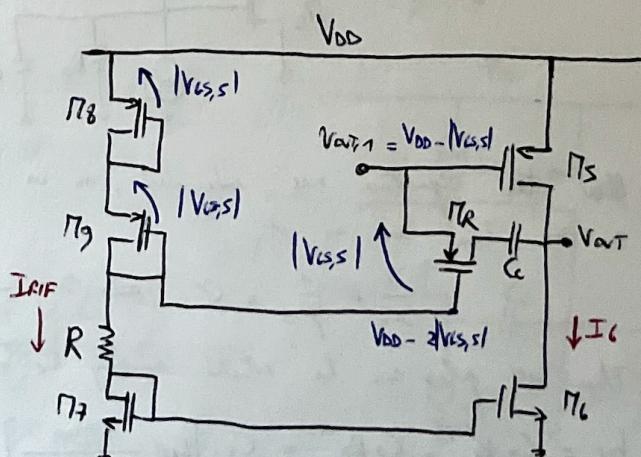[Just by chance is equal to the TRANSCONDUCTANCE of a MOSFET in saturation]



25


Voltage Buffer

This solution prevents the Miller effect, but kills the fast-forward path, $\approx \infty$ zero!

→ Ideal

The three capacitors are dependent, \approx we expect just two poles.

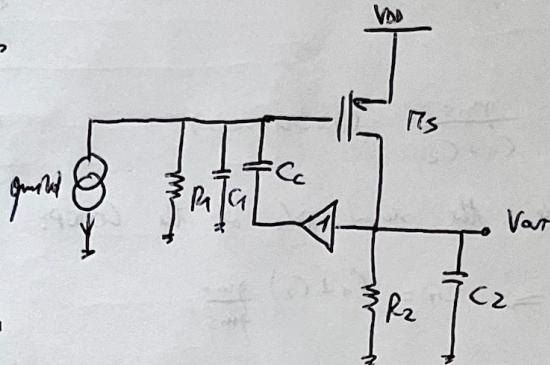The dominant pole is still due to the Miller effect





$$P_L = -\frac{1}{g_{mS} R_2 C_2 R_1}$$

The second pole can be avoided by connecting C_c or a short. C_1 is a \approx zero, while we have

$$P_H = -\frac{1}{C_2 \cdot \frac{1}{g_{mS}}} \quad (\text{higher, it doesn't depend on } C_1 !)$$

→ Real

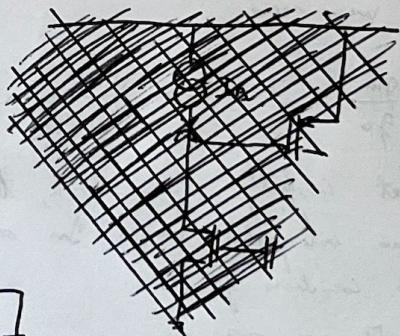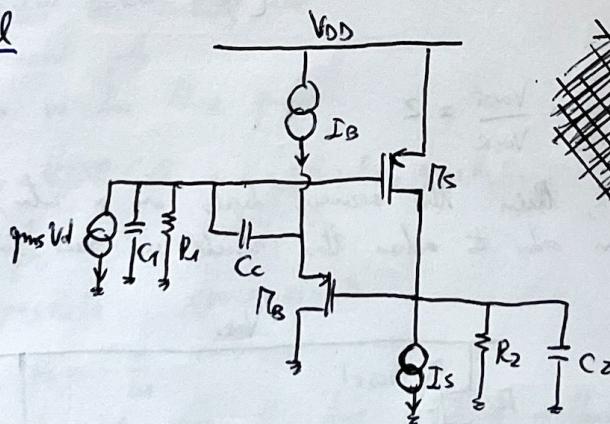

Now the capacitors are independent, so we have an additional HF pole and a \approx zero. The \approx zero is at

$$\frac{1}{2C_c} + \frac{1}{g_{mB}} = 0 \Rightarrow z = -\frac{1}{C_c \cdot \frac{1}{g_{mB}}} \quad (\text{output unit of } r_o \xrightarrow{\text{toward ground}})$$

The HF poles can be avoided avoiding C_c or a short

$$b_1 = C_1 R_1^{(c)} + C_2 R_2^{(c)} = C_1 \cdot \left[R_1 \parallel \frac{1/g_{mB}}{1+g_{mS} R_2} \right] + C_2 \cdot \left[\cancel{R_2} \frac{1}{1+g_{mS} R_2} \right] \approx \frac{C_2}{g_{mS}}$$

$$b_2 = C_1 C_2 R_1^{(0)} R_2^{(1)_{\text{DC}}} = C_1 C_2 \frac{R_2}{g_{mB} g_{mS} R_2} = \frac{C_1 C_2}{g_{mB} g_{mS}}$$

So we get


$$\left[\omega^2 \frac{C_1 C_2}{g_{mB} g_{mS}} + \omega \frac{C_2}{g_{mS}} + 1 \right] = 0$$

↓

$$W_0 = \sqrt{\frac{g_{mB} g_{mS}}{C_1 C_2}} \quad Q = \frac{g_{mS}}{C_2} \sqrt{\frac{C_1 C_2}{g_{mB} g_{mS}}} = \sqrt{\frac{g_{mS} C_1}{g_{mB} C_2}} \quad (\text{POLE PAIR})$$

• Ansatz

→ Real

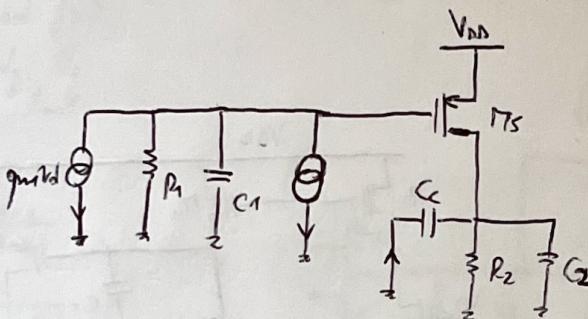

The Miller effect is still present ($V_C = g_{mS} i_S R_2$, $i_C = \omega C_C g_{mS} R_2 v_S$)
Same LF pole.

C_c and C_L are in \parallel , so only two poles are expected. We can short C_c or a short and compute the MF pole:

$$b_1 = G_2 \cdot 0 + G_1 \cdot \left(R_1 \parallel \frac{1}{g_{mS}} \right) \approx \frac{G}{g_{mS}}$$

$$P_M \approx -\frac{1}{C_1 \cdot \frac{1}{g_{mS}}} \quad (\text{load capacitance plays no role!})$$


→ Real

We have a LHP zero at

$$\frac{1}{2C_C} + \frac{1}{g_{mS}} = 0$$

$$\downarrow \quad z = -\frac{1}{C_C \cdot \frac{1}{g_{mS}}} \quad (\text{output shorted to ground})$$

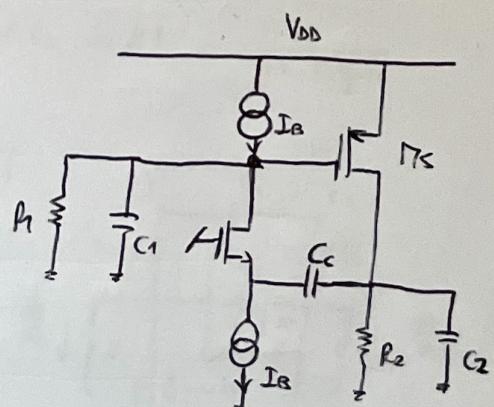and three poles. The LF pole is still due to the Miller effect, which we can reduce by shorting C_C :



(27)

$$b_1 = C_1 \cdot \left[R_1 \parallel \frac{1}{g_{ms}} \right] + C_2 \cdot R_2 \parallel \left(\frac{1/g_{ms}}{1+g_{ms}R_1} \right) \approx C_1 \frac{1}{g_{ms}}$$

$$b_2 = C_1 C_2 \cdot \frac{1}{g_{ms}} \cdot \frac{1}{g_{ms}}$$

So we get

$$\frac{C_1 C_2}{g_{ms}^2} s^2 + 2 \cdot \frac{C_1}{g_{ms}} + 1 = 0$$

$$W_0 = \sqrt{\frac{g_{ms}^2}{C_1 C_2}} \quad Q = \frac{g_{ms}}{C_1} \cdot \sqrt{\frac{C_1 C_2}{g_{ms}^2}} = \sqrt{\frac{C_2 g_{ms}}{C_1 g_{ms}}}$$

For the same C_2 , the Ahuja configuration has a higher Q factor than the voltage buffer configuration, as poles remain close and don't tend to split.


• ALTERNATIVE AHUJA (CASCODE)

Compute b_3, b_2, b_1 and a_2, a_1 and write

$$b_3 s^3 + b_2 s^2 + b_1 s + 1 = 0$$

$\Downarrow \approx$
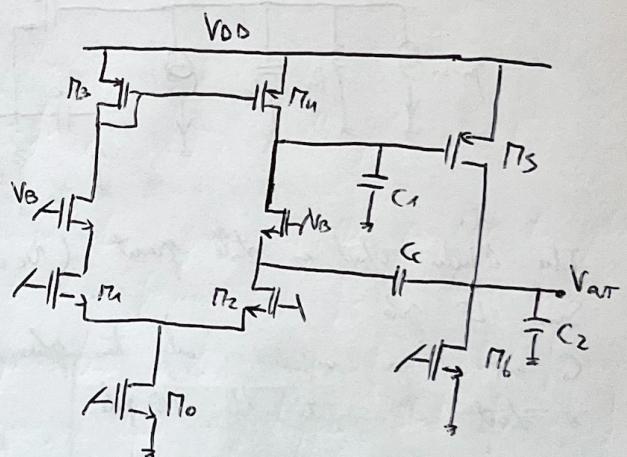
$$(1+b_1 s) \left(1 + \frac{b_2}{b_1} s + \frac{b_3}{b_1} s^2 \right) = 0$$



COMPENSATION (THREE-STAGE)

We use three-stage OTAs as this we need a large gain and do not have enough voltage headroom to accommodate cascades.

Now we have three high impedance nodes, so we need two separate Miller compensations.

① Place a Miller

capacitor across the third stage, in order to split f_2 and f_3 .

Let's consider only the cascade of the last two stages:


$$\text{LBW}P_{23} = \frac{g_m^2}{2\pi C'_c}$$

$$f'_3 = \frac{g_m^3}{2\pi(C_3 + C_2)}$$

$$f_2 = \frac{g_m^3}{2\pi C'_c} \quad (\text{POSITIVE})$$

Usually $g_m^3 \gg g_m^2$, so we can neglect f_2 .

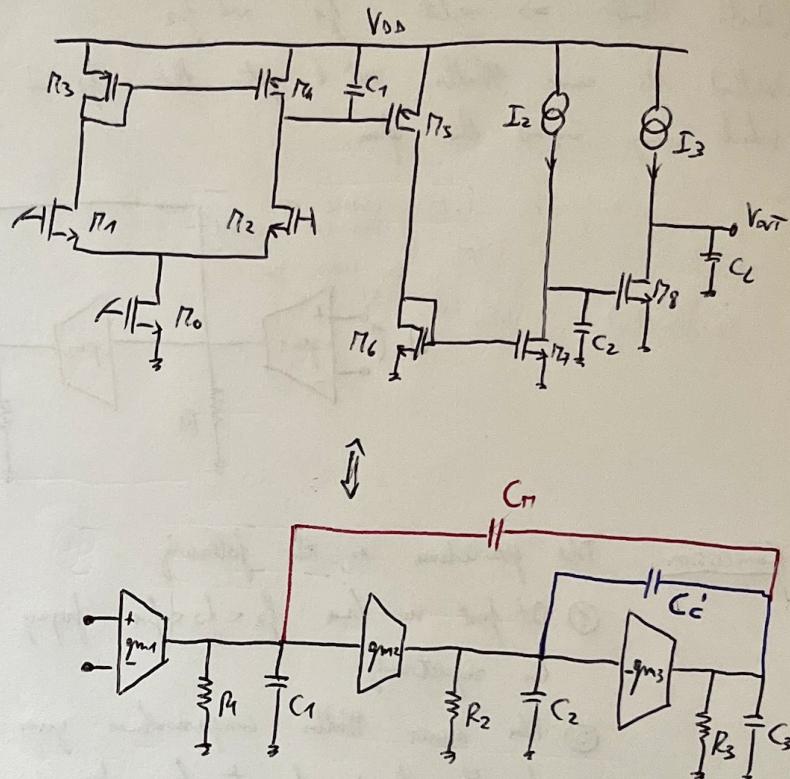Set g_m of the 2-3 stage by placing $f'_3 = 2 \text{ LBW}P_{23}$



② Place an outer Miller capacitor in order to further lower the frequency of the first pole

$$\text{GBWP} = \frac{g_m^1}{2\pi C_1}$$

The second pole can be shifted by shifting C_1 :

$$R_3^{(o)} = \frac{R_4/R_3}{1 + g_m^2 R_2 g_m^3 (R_4/R_3)} \quad (\text{seen by } C_1 \text{ and } C_3 \text{ in } ||) = \frac{1}{g_m^2 R_2 g_m^3}$$

$$R_2^{(o)} = \frac{R_2}{1 + g_m^2 R_2 g_m^3 (R_4/R_3)} \approx \frac{1}{g_m^2 g_m^3 (R_4/R_3)}$$

$$R_{cc}^{(o)} = \frac{1}{g_m^2} - \frac{1}{g_m^3}$$

$$\downarrow$$

$$= \frac{g_m^3 - g_m^2}{g_m^3 g_m^2}$$


$$\begin{cases} i_S = -g_m^2 V_2 \\ i_S = -g_m^3 V_1 \end{cases}$$

$$\Downarrow$$

$$V_1 = -\frac{i_S}{g_m^3}$$

$$V_2 = -\frac{i_S}{g_m^2}$$

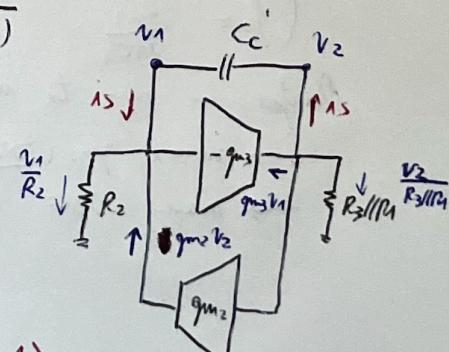
$$V_1 - V_2 = i_S \left(\frac{1}{g_m^2} - \frac{1}{g_m^3} \right)$$



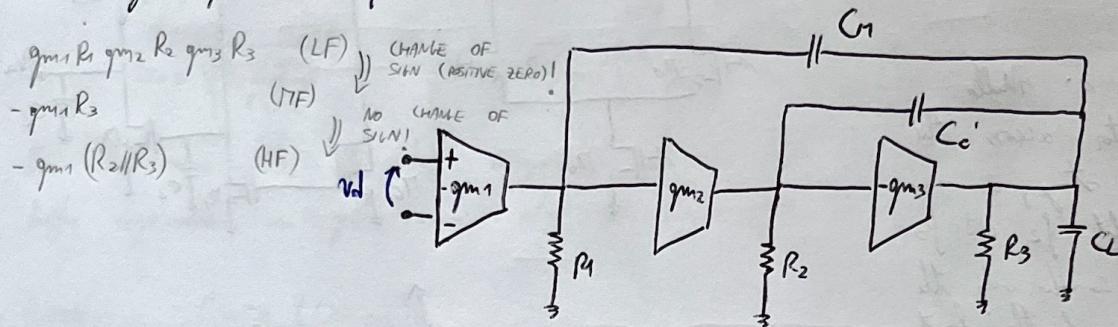(29) A better state of the regulators can be obtained if neglecting C_1 and C_2 , via the capacitated loads at the nodes are damped by the Miller compensation.

$\left\{ \begin{array}{l} \text{Inner Miller} \Rightarrow \text{pre-split } f_2 \text{ and } f_3 \\ \text{Outer Miller} \Rightarrow \text{split } f_1 \text{ and } f_2 \end{array} \right. \quad (\text{ROOT LOCUS})$

Without the inner Miller we'd get that f_2 and f_3 may have a pole gain, which may degrade the φ_m .



Conclusion: The procedure is the following:

- ① At first we have $f_3 < f_2 < f_1$ frequency of the poles due to C_3, C_2 and C_1 respectively
- ② The inner Miller compensation gives us the possibility to split f_3 and f_2 , thus bring f_2 to lower frequencies and f_3 to higher ones
- ③ The outer Miller compensation moves f_1 to lower frequencies and f_2 to higher frequencies, so there may happen that f_2 and f_3 move closer to each other and become a pole gain.

Neglecting the fact that the outer Miller compensation brings f_2 and f_3 closer to each other, we have that

$$\left\{ \begin{array}{l} GBWP \approx \frac{g_{m1}}{2\pi C_M} \\ f_2 \approx \frac{g_{m2}}{2\pi C_c} \quad (\approx \frac{1}{2\pi} \frac{1}{C_c \left[\frac{g_{m3} - g_{m2}}{g_{m2} g_{m3}} \right]}) \\ f_3 \approx \frac{g_{m3}}{2\pi C_3} \end{array} \right.$$

Therefore, in order to improve φ_m , we could either

→ increase g_{m2} (MORE POWER DISSIPATION) and g_{m3}

→ decreasing GBWP by moving C_1 (MORE SILICON AREA)

SINGLE-STAGE OTA

TELESCOPIC CASCADE

This structure has a cascade both on the upper and lower sides with respect to V_{AS} ,

$$\approx g_m h_{DT} \approx \frac{k^2}{2}$$

[DRAWBACK: reduced voltage swing]

$$\rightarrow V_{AS,max} = V_{DD} - V_{SG,3,8} - V_{ov,6}$$

note that we may improve it by using an ENHANCED MIRROR

$$\rightarrow V_{AS,min} = V_B - |V_T|$$

$$\rightarrow V_{AS,max} = V_B - V_{SG,4} + |V_T| = V_B - V_{ov}$$

$$\rightarrow V_{AS,min} = V_{ov,0} + V_{SG,1} = 2V_{ov} + |V_T|$$

Now, if we increase V_B we

INCREASE the common mode swing

DECREASE the output swing

and increase if we decrease V_B .





We have that

$$V_B,max = V_{DD} - V_{SG,2} - V_{ov,6} = V_{DD} - 2V_{ov} - |V_T|$$

$$V_B,min = V_{ov,0} - |V_T| + V_{ov,4} + |V_T| = 3V_{ov} + |V_T|$$

We may have two cases:

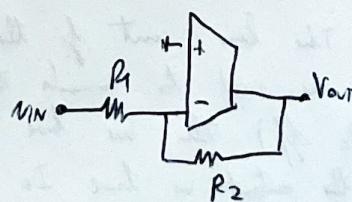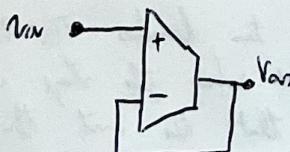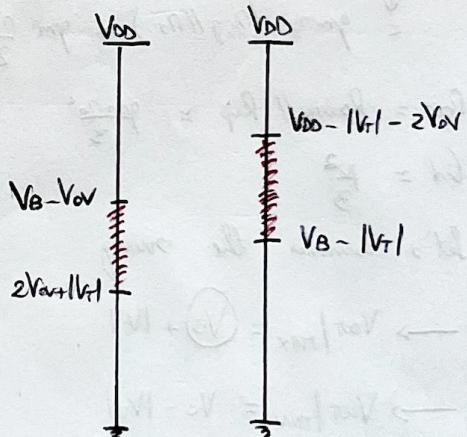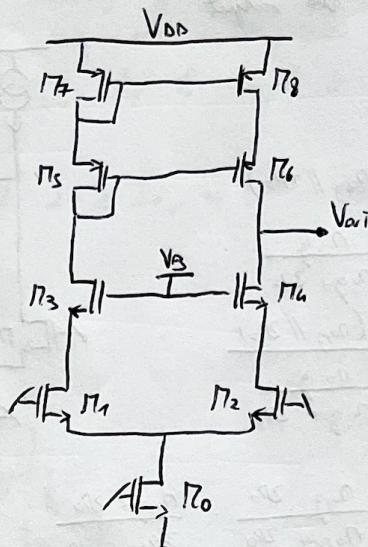- BUFFERS, we need the input and output swing to overlap as much as possible
- INVERTING CONFIGURATION, the virtual ground doesn't provide segments on the common mode range



31

FOLDED CASCADE

We avoid the series of many transistors in order to reduce voltage drop.
 Let's compute the output resistance:

$$R_{\text{down}} = g m \gamma_0^2$$

$$R_{\text{up}}^{(a)} = g_m n_0 (n_{\text{ag}} / 2 \pi)$$

$$\text{loop}(\theta) = - \frac{n_0 g}{n_0 g + 2n_0}$$

$$R_{sp} = \frac{g m r_0 (r_0 g / 2r_0)}{1 + \frac{r_0 g}{r_0 g + 2r_0}}$$

$$= g_m r_0 \frac{P_0 g - 2P_0}{P_0 g + 2P_0} \cdot \frac{P_0 g + 2P_0}{2P_0 g + 2P_0} =$$

$$\downarrow$$

$$= g_m r_0 (P_0 g / P_0) \approx g_m \frac{P_0^2}{2}$$

$$R_{\text{eff}} = R_{\text{outer}} // R_{\text{up}} \approx \frac{g m r_0^2}{3}$$

$$G_d = \frac{m}{R^2}$$

Let's consider the swing

$$\rightarrow \text{Var}_{\max} = V_3 + |V_1|$$

BIL DEAL

$$\rightarrow \text{Var}_{\text{min}} = V_c - |V_r|$$

$$\rightarrow V_{01} \Big|_{\max} = V_3 + |V_{SC,3}| + |V_4|$$

$$V_{\sigma_1} \mid_{MN} = V_{\sigma_0} + V_{\sigma_1} \pm (V_1 + 2V_0)$$

Note that by increasing V_B we increase both the current mode and the output swing.

$$V_{B/\text{max}} = V_{DD} - V_{\text{var},L} - |V_{CS,L}|$$


$$V_B|_{\pi N} = V_{\pi \bar{\pi}, MIN} - |V_T|$$

SLOW RATE PERFORMANCE

Let's consider the current of I_0 . The linear sum of the two branches $M_3 - M_4$ will be $I_C - I_0$. To set I_C we need to consider that when the loop is fully unbalanced (for example M_2 off) then we have that the current through M_3 will be $I_C - I_0$ and at the output we have I_0 .

32

If $I_L < I_0$, then M_3 and all the branch turns off, the potential of node (A) ^{decreases}
 until when M_1 and M_0 go ohmic, the matching $I_L = I_0$. On the M_4 branch instead,
 I_L increases the potential of the output node, then switching off M_4 , or driving it into ohmic in
 order to match the needed output current, the driving also I_L ohmic.
 In the very nodes (A) and (B) such voltages close to supply or ground, the charging
 the storage capacitors and driving down the circuit.
 Therefore, not to degrade the performances, we need $I_L \geq I_0$, no more power limitation.

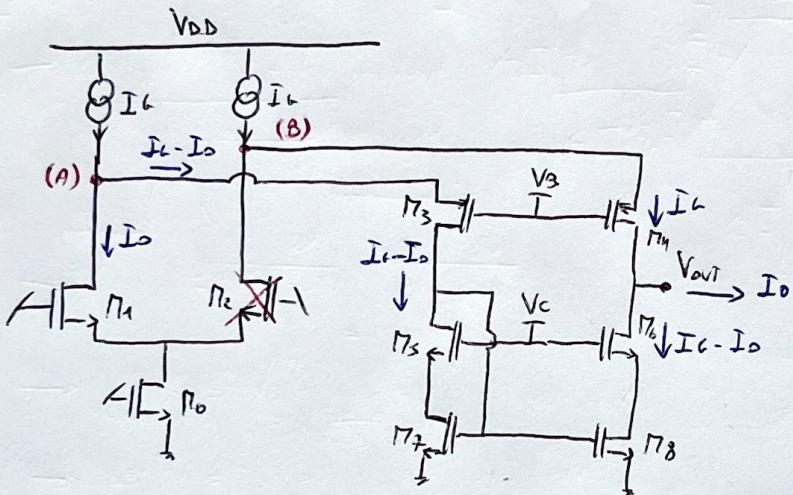

Variability And Matching

OMR and effect performances of a different amplifier are mainly affected by components' tolerances. They depend on material properties variability and on dimensional parameters variability.

→ RESISTORS

$$R = \frac{S}{W\Delta} L = R_0 \cdot \frac{L}{W} \quad R_0 \in [10 \Omega; 1 k\Omega]$$

$$\Delta R = \frac{L}{W} \Delta R_0 + \frac{R_0}{W} \Delta L + R_0 L \frac{\Delta W}{W^2} \quad (\text{We sum them up in abs to account for the worst case})$$

$$\frac{\Delta R}{R} = \frac{L}{W} \frac{\Delta R_0}{R_0} + \frac{R_0}{W} \frac{\Delta L}{L} + R_0 \cdot L \frac{\Delta W}{W}$$

Muchly negligible

We assume that S and Δ are subjected to variability over a characteristic spatial length $\Lambda \ll W, L$. From this condition, we can divide the resistors in elementary volumes of height Δ and area $A_0 = \Lambda \cdot \Lambda$. Each elementary volume will have a mean substitution of R_0 with \bar{R}_0 mean value and $\sigma(\bar{R}_0)$ standard deviation.

We can see the resistors as a matrix of $m \times n$ resistors, $m = \frac{L}{\Lambda}$ and $n = \frac{W}{\Lambda}$, each of them being a sample of a Gaussian distribution.

① ROWS $G_1 = \sum_{i=1}^N G_{1,i}$

$$E[G_1] = \sum_{i=1}^N E[G_{1,i}] = N \bar{R}_0$$

Now, being $G = \frac{1}{R}$ we may write


$$\frac{dG}{G} = \frac{dR}{R}, \Rightarrow \frac{\sigma^2(G)}{G^2} = \frac{\sigma^2(R)}{R^2}$$

assigning to R with small variances, in

order not to have PERCOLATIVE PATHS (high total variance, high variability)

$$\sigma^2(G_1) = \sum_{i=1}^N \sigma^2(G_{1,i}) = N \sigma^2(\bar{R}_0)$$
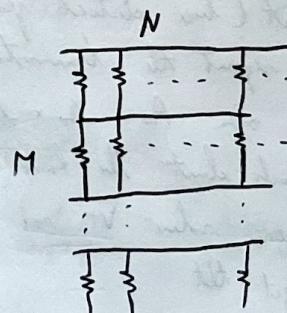
$$\frac{\sigma(G_1)}{G_1} = \frac{\sqrt{N} \sigma(\bar{R}_0)}{N \bar{R}_0} = \frac{\sigma(\bar{R}_0)}{\bar{R}_0} \cdot \frac{1}{\sqrt{N}} = \frac{\sigma(\bar{R}_0)}{\bar{R}_0} \cdot \frac{1}{\sqrt{N}} = \frac{\sigma(R_0)}{R_0}$$



② COLUMNS

$$R_{\text{row}} = \frac{1}{N \bar{R}_0} = \frac{\bar{R}_0}{N}$$

$$\frac{\sigma(R_{\text{row}})}{R_{\text{row}}} = \frac{\sigma(\bar{R}_0)}{\bar{R}_0} \cdot \frac{1}{\sqrt{N}}$$

34) So we get that the mean value of the total resistance is

$$\bar{R} = M \frac{\bar{R}_0}{N}$$

and the standard deviation is

$$\frac{\sigma(\bar{R})}{\bar{R}} = \frac{\sqrt{M \sigma^2(R_{\text{row}})}}{M \frac{\bar{R}_0}{N}} = \frac{\sigma(R_{\text{row}})}{\bar{R}_0} = \frac{\sigma(R_0)}{R_0} \cdot \frac{1}{\sqrt{MN}} = \frac{\sigma(R_0)}{R_0} \cdot \frac{\sqrt{M}}{\sqrt{WL}}$$

$$\Rightarrow \frac{\sigma(R)}{R} = \frac{M \sigma R}{\sqrt{WL}}$$

Let's consider now two nominally identical resistors R_1 and R_2 : if they are manufactured close to each other, the mismatch is mainly due to statistical variability, so we can write

$$\Delta R = \sigma(\Delta R) = \sqrt{\sigma^2(R_1) + \sigma^2(R_2)}$$

$$\frac{\sigma(\Delta R)}{\Delta R} = \sqrt{\frac{\sigma^2(R_1)}{R^2} + \frac{\sigma^2(R_2)}{R^2}} = \sqrt{\frac{2 \sigma^2(R)}{WL}} = \frac{\sqrt{2} \sigma R}{\sqrt{WL}} = \frac{M \sigma R}{\sqrt{WL}}$$

→ TRANSISTORS

As for resistors, also for transistors the variability due to threshold and conductivity coefficient (base electrical properties) are limited with respect to dimensional parameters.

Let's represent the transistors area into a matrix of $M \times N$ shorted transistors with area $A_0 = 1 \times 1$ in which the variability affects the V_T value.

For each short the local V_T is a sample extracted from a Gaussian distribution of mean value \bar{V}_T and standard deviation $\sigma(V_T)$

We get that

[The overall threshold is the average of all the average conductivities of each shorted area]

$$\bar{V}_T = E[E[V_{T,i}]] = \bar{V}_T = \frac{1}{M \cdot N} \sum_{i=1}^N \sum_{j=1}^M V_{T,j}$$

$$\sigma^2(\bar{V}_T) = E[(E[V_{T,i}])^2] = \frac{1}{(M \cdot N)^2} \cdot \sigma^2 \left(\sum_{i=1}^N V_{T,i} \right) = \frac{1}{(M \cdot N)^2} \cdot M \cdot N \cdot \sigma^2(V_{T,i})$$

$$\sigma(\bar{V}_T) = \sqrt{\frac{A_0}{W \cdot L} \sigma^2(V_{T,i})} = \frac{M \sigma}{\sqrt{WL}}$$

and, considering two nominally equal transistors,

$$\sigma(\Delta V_T) = \frac{\sqrt{2} M \sigma}{\sqrt{WL}} = \frac{M \sigma}{\sqrt{WL}}$$

$V_{T,i} \triangleq$ threshold of an shorted area
 $V_{T,0} \triangleq$ average threshold of an shorted area
 $\sigma(V_{T,0}) \triangleq$ standard deviation of an shorted area

CIRR

We can write, in general,

$$V_{out} = G_d V_d + G_m V_{cm} = G_d \left[V_d + \frac{G_m}{G_d} V_{cm} \right] = G_d \left[V_d + \frac{V_{cm}}{CMRR} \right]$$

so the common mode signal, together with the CMRR, is responsible for an output referred offset. Since CMRR depends on frequency, @ HF this effect contribution may be relevant.


Let's assume to have an input common mode signal at the input, it is almost entirely bypassed at this node, being thus follows:

$$i_{cm} = \frac{V_{cm}}{2R_{o,g}} \quad [\text{Common mode current flowing in the two branches}]$$

One to remember we may have that $i_{out} = \epsilon i_{cm}$, so

$$G_m = \frac{\epsilon R_{out}}{2R_{o,g}}$$
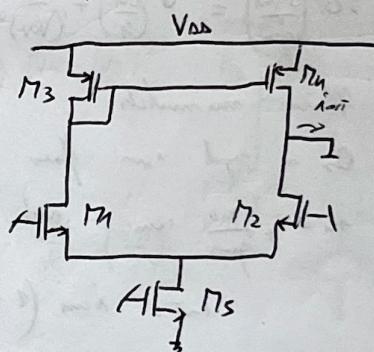
$$CMRR = \frac{gm_{ds} R_{out}}{\frac{\epsilon R_{out}}{2R_{o,g}}} = \frac{2gm_{ds} R_{o,g}}{\epsilon}$$



→ DETERMINISTIC ϵ

(1) Matching error

i_{cm} in the left-hand branch is partially lost into $R_{o,g}$ and not mirrored, thus causing



$$\epsilon = i_{cm} \frac{1/gm_{M1}}{\frac{1}{gm_{M1}} + R_{o,g}} = i_{cm} \frac{1}{1 + gm_{M1} R_{o,g}} \approx \frac{i_{cm}}{gm_{M1} R_{o,g}}$$

(2) Unbalanced resistances at the output pair's drain nodes

$$R_{S,1} = \frac{\frac{1}{gm_{M1}} + R_{o,D}}{1 + gm_{ds} R_{o,D}} =$$

$$R_{S,2} = \frac{\frac{R_{o,D}}{gm_{M2}}}{\frac{1}{gm_{M2}} + R_{o,D}} = \frac{R_{o,D}}{1 + gm_{ds} R_{o,D}}$$

$$\epsilon i_{cm} = 2i_{cm} \frac{R_2}{R_1 + R_2} - 2i_{cm} \frac{R_1}{R_1 + R_2} = \frac{R_2 - R_1}{R_2 + R_1} 2i_{cm} = \frac{\frac{1}{gm_{M1}}}{2R_{o,D} + \frac{1}{gm_{M1}}} 2i_{cm}$$

$$R_2 - R_1 = -\frac{1}{gm_{M1}}$$

$$R_2 + R_1 = \frac{2R_{o,D} + \frac{1}{gm_{M1}}}{1 + gm_{ds} R_{o,D}}$$

(36)

$$\text{iam } \Sigma \approx \frac{1}{2\rho_{0,D} g_{m,11}} \cdot 2 \text{iam} = \frac{1 \text{iam}}{\rho_{0,D} g_{m,11}}$$

$$\Rightarrow \left[\Sigma_{\text{DET}} \approx \frac{1}{\rho_{0,D} g_{m,11}} + \frac{1}{\rho_{0,T} g_{m,11}} \right]$$

→ STATISTICAL OVR

$$dgm = d(2 \text{iam}) = 2 d\text{iam} + 2 dV_T$$

$$\frac{dgm}{gm} = \frac{dk}{k} + \frac{dV_T}{V_T}$$

Assume that Δk and ΔV_T are statistically independent (they are not) we get

$$\sigma^2 \left(\frac{\Delta gm}{gm} \right) = \sigma^2 \left(\frac{\Delta k}{k} \right) + \frac{1}{(V_T)^2} \sigma^2 (\Delta V_T)$$

[Because for example a variation of V_T multiplies C_{ox} , which is present both in k and V_T formulae]

① Mirror mismatch

On a rigid iam flows into N_3 , $i_{N_3} = - \frac{1 \text{iam}}{gm_3}$, then we get

$$i_k = + \frac{gm_6}{gm_3} \text{iam} \quad \text{and so}$$

$$i_{\text{out}} = \text{iam} \left(1 - \frac{gm_6}{gm_3} \right) = \frac{gm_3 - gm_6}{gm_3} \text{iam} \approx \frac{\Delta gm_6}{gm_6} \text{iam}$$


so

$$\Sigma_m^{(\text{STAT})} \approx \frac{\Delta gm_6}{gm_6}$$

② Input mismatch

We need i_{N_5} , so we fold one transistor on the other
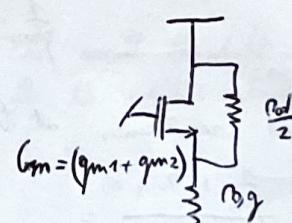
$$\begin{aligned} i_5 &= \text{iam} \cdot \frac{\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2}}{\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} + \frac{1}{2gm}} \\ &\downarrow \\ &= \text{iam} \cdot \frac{2gm_5 \left(\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} \right)}{1 + 2gm \left(\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} \right)} \end{aligned}$$



$$i_2 - i_1 = i_{\text{out}} = \text{iam} \cdot \frac{(gm_1 - gm_2)}{1 + 2gm \left(\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2} \right)}$$

$$\downarrow \\ \approx \frac{\Delta gm_6}{2gm_6} \cdot \frac{\frac{\rho_{0,g}}{2} + \frac{\rho_{0,D}}{2}}{\frac{\rho_{0,g}}{2} / \frac{\rho_{0,D}}{2}} \text{iam} = \frac{\Delta gm_6}{gm_6} \frac{\text{iam}}{2gm} \left(\frac{\rho_{0,g}}{\rho_{0,D}} + \frac{\rho_{0,D}}{\rho_{0,g}} \right)$$

$$\Rightarrow \Sigma_D^{(\text{STAT})} = \frac{\Delta gm_6}{gm_6} \left(\frac{2\rho_{0,g}}{\rho_{0,D}} + 1 \right)$$

For $\rho_{0,g} \rightarrow +\infty$ we get OVR → $\frac{2gm_6 \rho_{0,D}}{\left(\frac{\Delta gm_6}{gm_6} \right) \frac{\rho_{0,D}}{\rho_{0,g}}} = \frac{gm_6 \rho_{0,D}}{\left(\frac{\Delta gm_6}{gm_6} \right)}$

OFFSET

In a single-ended OTA, in principle, the output voltage should be at $\frac{V_{DD} - V_{EE}}{2}$ if no differential signal drives the two inputs. If the parameters varied deviate from nominal values, we may have that $V_{OS} \neq \frac{V_{DD} - V_{EE}}{2}$, thus causing an output voltage offset. We usually describe the output as an ideal one with an offset equivalent current placed between the output terminals, when

$$V_{OS} = \frac{V_{OS,DS}}{I(D)}$$


Minibias between transistors of the input stage are more critical, being thus amplified by the total gain of the stage.

$$\rightarrow \frac{k \text{ mismatch}}{I_1 \delta I_2}$$

$$I_1 = \left(k + \frac{\Delta k}{2} \right) (V_{GS} - V_T)^2 ; \quad I_2 = \left(k - \frac{\Delta k}{2} \right) (V_{GS} - V_T)^2$$

$$|\Delta I| = |\Delta k (V_{GS} - V_T)^2| = |I_1 - I_2|$$

$$V_{OS/km} = \frac{|\Delta I|}{gm} = \frac{V_{os}^2 \Delta k}{gm} = \frac{V_{os}^2 \cdot \Delta k}{2k \cdot V_{os}} = \frac{\Delta k}{k} \cdot \left(\frac{V_{os}}{2} \right)$$

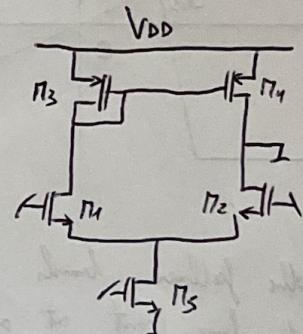

$$\rightarrow \frac{V_T \text{ mismatch}}{I_1 \delta I_2}$$

$$I_1 = k \left(V_{GS} - V_T - \frac{\Delta V_T}{2} \right)^2 ; \quad I_2 = k \left(V_{GS} - V_T + \frac{\Delta V_T}{2} \right)^2$$

$$|\Delta I| = \left| k \left[\left(V_{GS} - V_T \right)^2 + \frac{\Delta V_T^2}{4} - 2V_{os} \cdot \frac{\Delta V_T}{2} - \left(V_{GS} - V_T \right)^2 + \left(\frac{\Delta V_T^2}{4} \right) - 2V_{os} \cdot \frac{\Delta V_T}{2} \right] \right| = 2k V_{os} \cdot \Delta V_T$$

$$V_{OS/\Delta V_T} = \frac{|\Delta I|}{gm} = \frac{2k V_{os}}{2k V_{os}} \cdot \Delta V_T = \Delta V_T$$

$$\rightarrow \frac{k \text{ mismatch}}{I_3 \delta I_4}$$

$$I_3 = \left(k_m + \frac{\Delta k_m}{2} \right) (V_{GS} - V_T)^2 ; \quad I_4 = \left(k_m - \frac{\Delta k_m}{2} \right) (V_{GS} - V_T)^2$$

$$|\Delta I| = 2 \frac{\Delta k_m}{2} (V_{GS} - V_T)^2$$

$$V_{OS/\Delta k_m} = \frac{|\Delta I|}{gm} = \frac{\Delta k_m}{2k_D \cdot V_{os}} V_{os}^2 = - \frac{\Delta k_m V_{os, m}^2}{2I} V_{os,D} = \frac{V_{os,D}}{2} \left(\frac{\Delta k_m}{k_m} \right)$$

$$\rightarrow \frac{V_T \text{ mismatch}}{I_3 \delta I_4}$$

$$I_3 = k_m \left(V_{GS} - V_T - \frac{\Delta V_T}{2} \right)^2 ; \quad I_4 = k_m \left(V_{GS} - V_T + \frac{\Delta V_T}{2} \right)^2$$


38

$$|\Delta I| = 2k_m V_{os,M} \cdot \Delta V_T$$

$$V_{os}|_{AVT} = \frac{2k_m V_{os,M}}{g_m} \Delta V_T = \frac{2k_m V_{os,M}}{2I} \cdot V_{os,D} \cdot \Delta V_T = \frac{2I}{V_{os,M}} \cdot \frac{V_{os,D} \Delta V_T}{2I} = \frac{V_{os,D}}{V_{os,M}} \Delta V_T$$

$$\Rightarrow \sigma^2(V_{os}) = \sigma^2(\Delta V_T) + \sigma^2(\Delta V_{os,D}) \left(\frac{V_{os,D}}{V_{os,M}} \right)^2 + \left[\sigma^2\left(\frac{\Delta V_T}{V_{os,D}}\right) + \sigma^2\left(\frac{\Delta V_{os,D}}{V_{os,D}}\right) \right] \left(\frac{V_{os,D}}{2I} \right)^2$$

Offset is compensated by FEEDBACK:

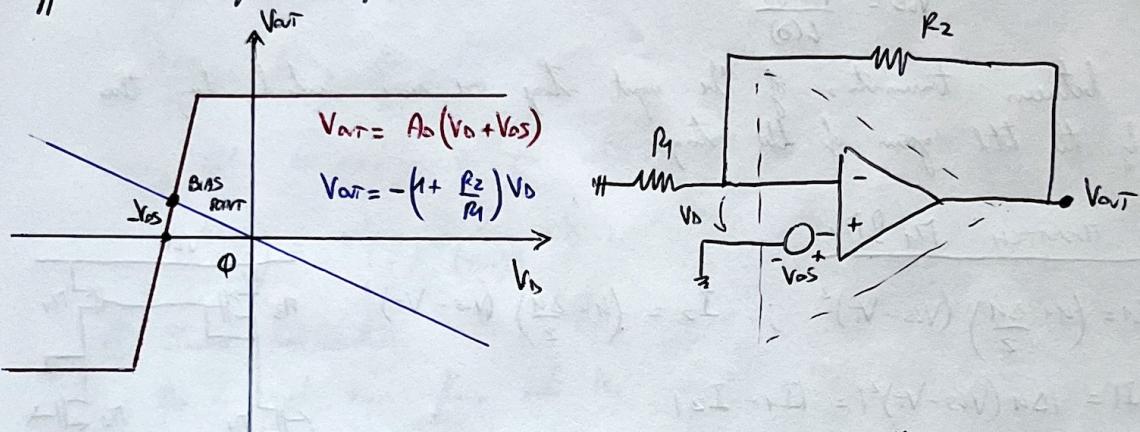

the feedback branch introduces a new relationship in the system, this setting the bias point at a value lower than the power supply. In order to have this situation, it must be

$$(1 + \frac{R_2}{R_1}) \ll A_o$$

↓

$$A_o \frac{R_1}{R_1 + R_2} \gg 1$$

$A_o \frac{R_1}{R_1 + R_2}$

[Therefore in order to properly act on the feedback nodes, the loop gain must be properly wired and $\gg 1$.]


Output Stages

→ Class - A (Transistors Are Always Active)

The right buffer stage is the source follower, where we set the output node at $V_{DD} - V_{EE}$ in order not to have a current into R_L when no input signal is applied ($V_{REF} = \frac{V_{DD} - V_{EE}}{2}$)

Let's assume to have a positive signal at the gate of M_7 . The gain of the stage is:
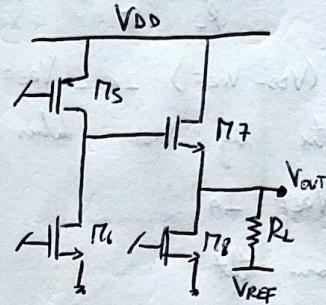
$$\frac{V_{OUT}}{V_{G,7}} = \frac{R_L}{R_L + \frac{1}{g_{m,7}}}$$



where $g_{m,7}$ is NOT constant, since it depends on the current value.

As $V_{G,7} \uparrow$, the current $I_7 \uparrow$, so $g_{m,7} \uparrow$ and overall $\left(\frac{V_{OUT}}{V_{G,7}}\right) \uparrow$. On the negative swing instead, $I_7 \downarrow$ and M_7 may turn off. In order to avoid the output clipping we need to have

$$R_L \cdot I_8 \geq \Delta$$

being Δ the peak (negative) voltage at the output.

This stage is also adopted in power AMPLIFIERS, as we may compute the

$$\text{POWER EFFICIENCY } \eta = \frac{V_p^2 / 2R_L}{I_8 V_{DD}} \stackrel{\Delta}{=} \frac{\text{POWER DELIVERED TO THE LOAD}}{\text{AVERAGE POWER DRAWN FROM SUPPLY}}$$

assuming that no clamping takes place, and that

$$\begin{cases} V_{DD} = 2V_{REF} \\ V_p \leq V_{REF} \end{cases}$$

$$\Rightarrow \eta \leq \frac{V_{REF}^2}{2R_L I_8 2V_{REF}} \leq \frac{V_{REF}^2}{4 \cdot V_{REF} \cdot V_{REF}} = \frac{1}{4}$$

→ Class - B (Push - Pull)

In order to avoid static power consumption, we may substitute the current generator with a pmos follower, so that

- on the positive swing the nmos turns on while the pmos is off
- on the negative swing the pmos turns on while the nmos is off
- for $-V_T \leq V_{G,7} - V_{REF} \leq V_T$ we have a dead zone that causes Crossover Distortion

therefore we have MORE DISTORTION, but BETTER POWER EFFICIENCY.

- (40) • The power delivered to the load is again $\frac{V_p^2}{2R_L}$ mighty distortion
- On the positive swing a current flows from V_{DD} to V_{REF} , whose mean value is
- $$I_A = \frac{1}{T/2} \int_0^{T/2} \frac{V_p}{R_L} \sin\left(\frac{2\pi}{T}t\right) dt = \frac{V_p}{R_L} \cdot \frac{2}{T} \frac{T}{2\pi} \cdot \left[\cos\left(\frac{2\pi}{T}t\right)\right]_0^{T/2}$$
- $$= \frac{V_p}{R_L} \cdot \frac{1}{\pi} \cdot 2 = \frac{2}{\pi} \frac{V_p}{R_L}$$

$$\Rightarrow \bar{P} = (V_{DD} - V_{REF}) \cdot I_A = V_{REF} \cdot I_A$$

On the negative swing V_{REF} delivers the same current towards ground, so again

$$\bar{P} = V_{REF} \cdot I_A.$$

Remembering again that

$$\begin{cases} V_p \approx V_{REF} \\ V_{DD} = 2V_{REF} \end{cases}$$



$$\eta \leq \frac{\frac{V_{REF}^2}{2R_L}}{V_{REF} \cdot 2 \cdot \frac{V_{REF}}{\pi} \cdot \frac{V_{REF}}{R_L}} = \frac{\pi}{4} \approx 78\%$$

We have that across each transistor

$$\begin{cases} V_{DS,max} = 2V_{REF} \\ I_{DSK} = \frac{V_{REF}}{R_L} \end{cases} \quad (\text{neglecting the overdrive})$$

$$P(t) = \frac{V_{REF}}{R_L} \sin(\theta) V_{REF} \left[1 - \sin(\theta) \right]$$
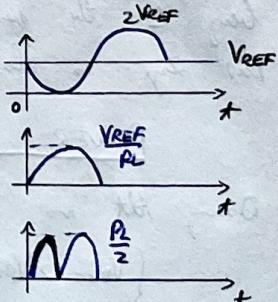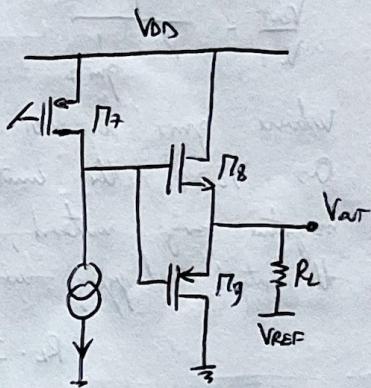
$$P_{max} = \frac{V_{REF}^2}{4R_L} \quad \left[\theta = \frac{\pi}{6} \right] \quad \left(\text{half of the maximum power delivered to the load!} \right)$$



→ CLASS A-B

To limit distortion due to the dead-zone of the push-pull stage, we shall bias the transistors M8 and M9 at the edge of their full conduction.



We may implement this voltage shifter by using a diode:

$$V_{GS,7} + V_{GS,8} = V_{GS,9}$$

$$\sqrt{\frac{I_7}{k_7}} + V_{T,IN} + \sqrt{\frac{I_7}{k_2}} + V_{T,P} = \sqrt{\frac{I_8}{k_8}} + V_{T,IN} \Rightarrow I_7 = \left(\frac{\sqrt{I_8/k_8} - V_{T,P}}{\sqrt{I_8/k_8} + \sqrt{I_7/k_7}} \right)^2$$

{DEPENDENT ON ABSOLUTE VALUES (BAD)!}

42

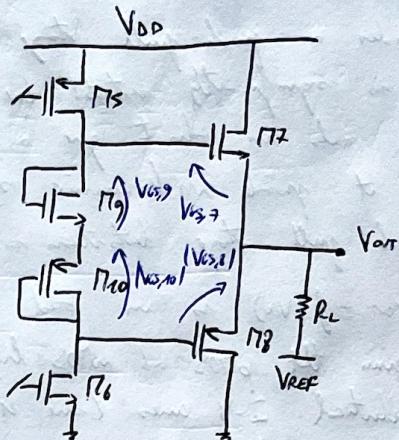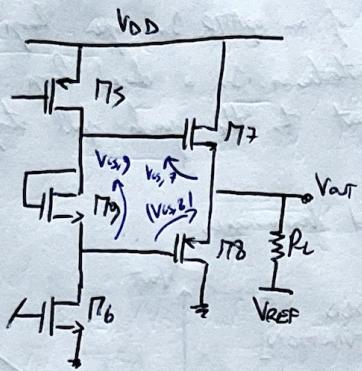

We may use the TRANSLINEAR PRINCIPLE by adding the complementary transistors, in such a way that the NBL in the $M_7 - M_8 - M_9 - M_{10}$ loop is depending only on V_{GS} terms and we can control more easily the currents.

$$\sqrt{\frac{I_7}{k_7}} + \sqrt{\frac{I_7}{k_8}} + V_{Tn} + V_{Tp} = \sqrt{\frac{I_9}{k_9}} + \sqrt{\frac{I_9}{k_{10}}} + V_{Tn} + V_{Tp}$$

$$\downarrow \\ I_7 = I_C \left(\frac{\sqrt{1/k_9} + \sqrt{1/k_{10}}}{\sqrt{1/k_7} + \sqrt{1/k_8}} \right)^2$$

So we can properly tailor the current (static one) in M_7 and M_8 by using the transistors M_9 and M_{10} .


$\begin{cases} \text{BIAS OF THE OUTPUT STATE} \Rightarrow \text{not by } R_{L\min} \text{ (avoid clipping)} \\ \text{SIZES OF } M_9 \text{ AND } M_{10} \Rightarrow \text{not by } I_2 \end{cases}$

DISTORTION AND FEEDBACK

Let's consider a push-pull stage or output stage of an opAMP. In open-loop operation, the output is significantly distorted due to crossover distortion. In a closed loop configuration, the feedback acts in such a way to give a pre-distorted signal to the push-pull stage and thereby minimize harmonic signals.

In a push-pull stage distortion is dominated by odd harmonics:

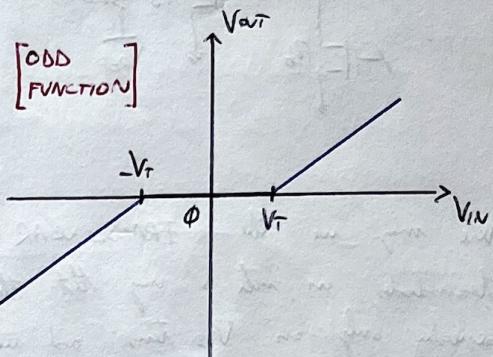→ $V_{out} = f(V_{in})$ is an odd function,
given that pMOS and nMOS have
identical I-V curves (same n
and same V_T)



→ if we drive the stage with


$$v_{in} = A_0 \sin(\omega t)$$

the signal out though T_{L2} is a replica of the signal out though T_{L1}
but with a $\frac{1}{2}$ shift, $\approx (\pi = \frac{2\pi}{\omega T})$

$$i_1(t) = A_0 + A_1 \sin(\omega_1 t + \phi_1) + A_2 \sin(\omega_2 t + \phi_2) + A_3 \sin(\omega_3 t + \phi_3) + \dots$$



$$i_2(t) = A_0 + A_1 \sin(\omega_1 t + \phi_1 + \pi) + A_2 \sin(\omega_2 t + \phi_2 + 2\pi) + A_3 \sin(\omega_3 t + \phi_3 + 3\pi) + \dots$$
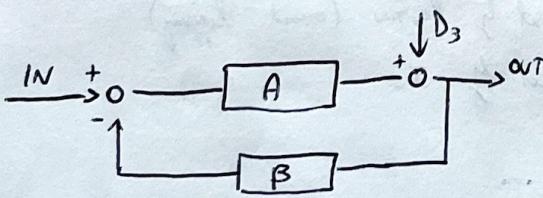
$$i_L = i_1 - i_2 = 2A_1 \sin(\omega_1 t + \phi_1) + 2A_3 \sin(\omega_3 t + \phi_3) + \dots$$




$$\text{PRE-DISTORTION} \\ -D_3^{out} \cdot A \cdot \beta + D_3 = D_3^{out}$$
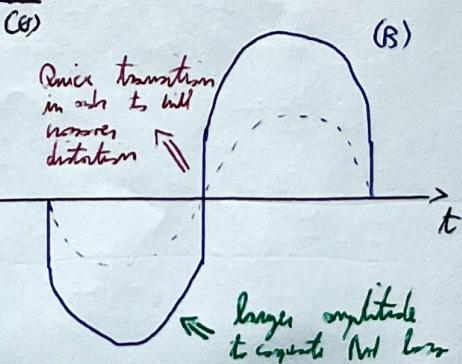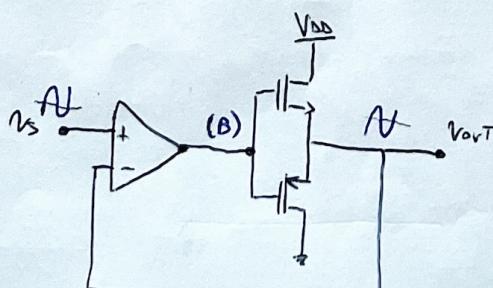
$$D_3^{out} = \frac{D_3}{1 + A\beta} \Rightarrow \frac{D_3^{out}}{D_3} = \frac{1}{1 + \text{loop gain}}$$



In-Band Zero-Pole Doublets

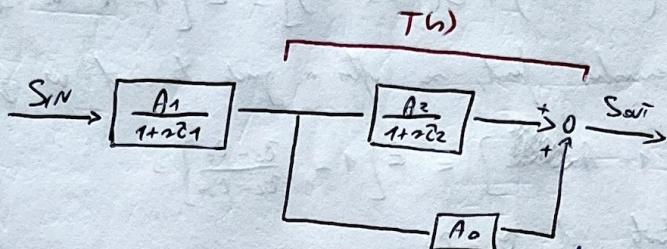In-band zero-pole doublets appear any time we need for example to drive a large load capacitance with a unity-gain compensated OTA stage, or when we use a FEED-FORWARDS compensation technique:



$$T(s) = \frac{A_2}{1+zC_2} + A_0 = \frac{1 + z \left(\frac{A_0 C_2}{A_2 + A_0} \right)}{1 + zC_2} (A_2 + A_0)$$

↳ In-pass blocks with broad band and low gains (BWP trade-off)

so we get a zero $\Rightarrow z_2 = \frac{A_0}{A_2 + A_0} z_2 < z_2$ ($\Rightarrow f_2 > f_z$).

These doublets increase Q_m but worsen the transient response of the amplifier.
Let's consider

$$A(s) = \frac{A_0 (1 + zC_2)}{(1 + zC_0)(1 + zC_p)} \quad (\text{T.F. of a unity-compensated OTA})$$

and $z_p < z_2 < z_0$. The closed-loop T.F. in a buffer configuration will be

$$H(s) = \frac{(1 + zC_2)}{(1 + zC_L)(1 + zC_M)}$$

Let's consider the response to a step function E


$$V_{out}(s) = \frac{E}{s} H(s)$$



$$= \frac{E}{s} \frac{1 + zC_2}{(1 + zC_L)(1 + zC_M)}$$


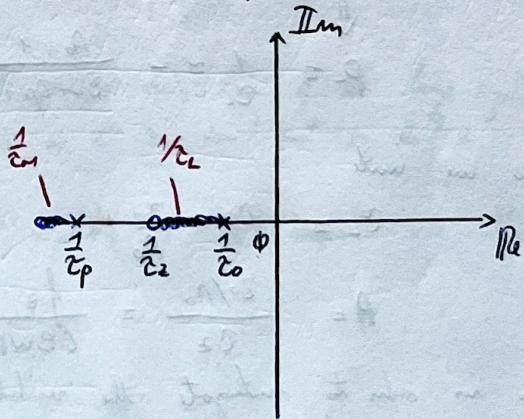
$$= \frac{E}{s} \left[\frac{A}{1 + zC_L} + \frac{B}{1 + zC_M} \right]$$



where

$$A = \lim_{s \rightarrow -\frac{1}{z_2}} H(s) (1 + zC_L) = \frac{1 + z_2 \left(-\frac{1}{z_L} \right)}{1 + z_2 \left(-\frac{1}{z_L} \right)} = \frac{z_L - z_2}{z_L - z_M}$$

$$B = \lim_{s \rightarrow -\frac{1}{z_M}} H(s) (1 + zC_L) = \frac{1 + z_2 \left(-\frac{1}{z_M} \right)}{1 + z_2 \left(-\frac{1}{z_M} \right)} = \frac{z_M - z_2}{z_M - z_L}$$

44

We get that

$$H(t) = \frac{A}{Z_L} e^{-\frac{t}{Z_L}} + \frac{B}{Z_H} e^{-\frac{t}{Z_H}}$$

so, by integration, we get:

$$\text{var}(t) = E \left[A \left(1 - e^{-\frac{t}{Z_L}} \right) + B \left(1 - e^{-\frac{t}{Z_H}} \right) \right] = E \left[1 - Ae^{-\frac{t}{Z_L}} - Be^{-\frac{t}{Z_H}} \right]$$

The first exponent vanishes first, so after a quick transit we get

$$\text{var}(t) \approx E \left[1 - Ae^{-\frac{t}{Z_L}} \right] = E \left[1 - \frac{Z_L - Z_p}{Z_L - Z_H} \right] =$$

We need an estimate of $Z_L - Z_p$:

$$(loop(s)) = -A_0 \frac{1 + r Z_p}{(1 + r Z_o)(1 + r Z_p)}$$

$$-(loop(s)) + 1 = 0$$

↓

$$-A_0 - A_0 Z_p \cdot r = 1 + r Z_o + r Z_p + r^2 Z_o Z_p$$

↓

$$r^2 Z_o Z_p + r(Z_o + Z_p + A_0 Z_p) + A_0 + 1 = 0$$

↓

$$P_L = -\frac{1}{Z_L} \approx -\frac{A_0 + 1}{Z_o + Z_p + A_0 Z_p} = -\frac{1}{Z_p + \frac{Z_o}{A_0}} \quad (\text{big } Z_o \gg Z_p)$$

So we write

$$Z_L = Z_p + \frac{Z_o}{A_0}$$


$$A = \frac{Z_o / A_0}{Z_L} = \frac{f_z}{GBWP}$$

so in order to mitigate the residual gain that has to be coped with the slow time constant, we must shift f_z to LF, but this must also to share Z_L even down!

For the case of feed-forward compensation, $Z_o > Z_p > Z_L$ so the net loss is different and we expect

$$Z_L < Z_p$$

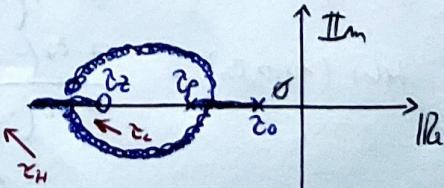so the response has an overshoot that is then removed with the slow time constant Z_L



SLEW RATE


(45)

The slew-rate performance is related to the power available to charge capacitors.

If we consider a large input signal for example I_{13} at fully nonlinearities the differential signals, thus mostly $I_{11} - I_{13} = I_{14}$ off and little I_{11} flows into C_c . As a result, $V_{c,s}$ ↓ and I_{15} comes

$$I_s + \Delta I_s$$

$$\frac{2I_o}{C_c}$$

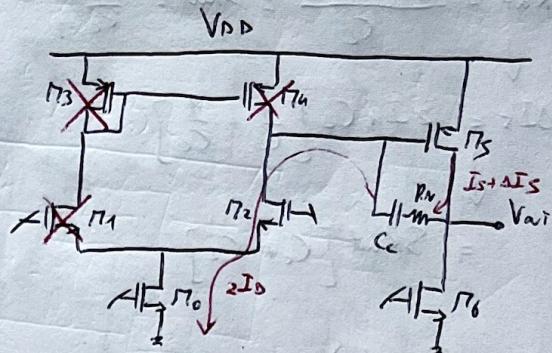

The initial response is a linear ramp with $SR = \frac{I_o}{C_c}$. If we come to have the OTA in a buffer configuration, then we recover the expected behavior when

$$\left\{ \begin{array}{l} SR = \frac{\Delta V}{2} \\ \Delta V = V_{(00)} - SR \cdot t_{SLEW} \\ \downarrow \\ \left\{ \begin{array}{l} \Delta V = SR \cdot z \\ t_{SLEW} = \frac{V_{(00)}}{SR} - z \end{array} \right. \end{array} \right.$$

$$\Rightarrow V_{out}(t) = \begin{cases} SR \cdot t & (t \leq t_{SLEW}) \\ V_{(00)} - \Delta V \cdot e^{-\frac{(t-t_{SLEW})}{z}} & (t \geq t_{SLEW}) \end{cases}$$

This discussion is valid under the assumption that the ring bias of the large input signal is $< \frac{z_L}{G(s)} = \frac{1}{GBWP(OTA)}$ of the OTA, so that V_{out} doesn't reach to the large input at first.

If we consider an harmonic signal instead, whose amplitude is the maximum one allowed by the output dynamics, then

$$2\pi f_{max} \text{ Amplitude} = \frac{dV_{out}}{dt} \Big|_{max} \leq SR$$

$$f_{max} \leq \frac{SR}{2\pi T_{max}} \stackrel{D}{=} \underline{\text{POWER BANDWIDTH}}$$

Finally, we can point out that

$$SR = \frac{I_o}{C_c} = \frac{V_{out,1} \cdot g_m,1}{C_c} = 2\pi V_{out,1} \cdot GBWP$$

[one GBWP is not, we need to mean $V_{out,1}$ in order to mind SR, but the \leftrightarrow symbol E_{in}^2]

EXTERNAL SR

Let's consider now a load capacitance. We must distinguish now two cases

① Large V_p (positive)

$I_{11} - I_{13} - I_{14}$ are off and $2I_1$ flows into C_c . Under the assumption that V_A reaches a steady state, the ~~ring~~ ramp rate across C_c can't be equal to the

(46) one across C_L , being it equal to $S_{Rout} = \frac{2I_1}{C_L}$ imposed by the first stage, so it must be


$$S_{Rout}^+ = \frac{\Delta I_S - 2I_1}{C_L} = S_{Rout} = \frac{2I_1}{C_L}$$

$$\downarrow$$

$$\Delta I_S = 2I_1 C_L \left[\frac{1}{C_L} + \frac{1}{C_C} \right]$$

$$\downarrow$$

$$= S_{Rout} [C_C + C_L]$$

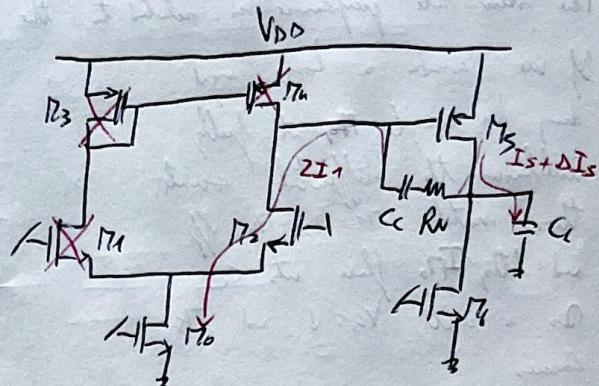

② V_P large (negative)

M_2 off, $2I_1$ flows into $M_1 - M_3 - M_4$, M_5 's count decreases

$$S_{Rout}^- = \frac{\Delta I_S - 2I_1}{C_L} = S_{Rout} = \frac{2I_1}{C_L} \quad (\text{if } S_{Rout} \text{ is now limited by the output load})$$

$$\downarrow$$

$$\Delta I_S = 2I_1 C_L \left[\frac{1}{C_L} + \frac{1}{C_C} \right] = S_{Rout} (C_L + C_C)$$


But if $\Delta I_S > I_S$, then M_5 turns off and M_6 has to bias both C_C and C_L . In this case, at steady state the charge rate across C_C matches the one across C_L , so

$$\frac{I_6 - I_4}{C_L} = \frac{I_6}{C_C} = S_{Rout}^-$$

\downarrow

$$\begin{cases} I_4 = I_6 \cdot \frac{C_C}{C_L + C_C} < 2I_0 \\ S_{Rout}^- = \frac{I_6}{C_L + C_C} \end{cases}$$

then I_4 drops!

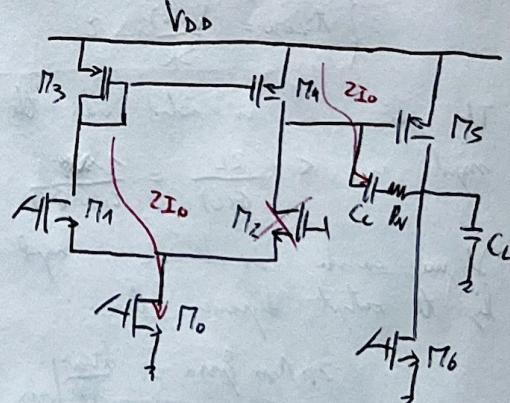

In this w

$$S_{Rout} = \min \left\{ S_{Rout} ; \frac{I_6}{C_L + C_C} \right\}$$

Has to have that S_{Rout} is the limiting one on both polarities?


→ instead I_6

→ use a class A-B, raise M_6 count only when needed!


LASS AB Source For Slew Rate

$M_2 - M_3$ act as voltage shifter to properly set M_6 's bias. We mix them in order to provide a shift of $0.8V + 0.8V$.

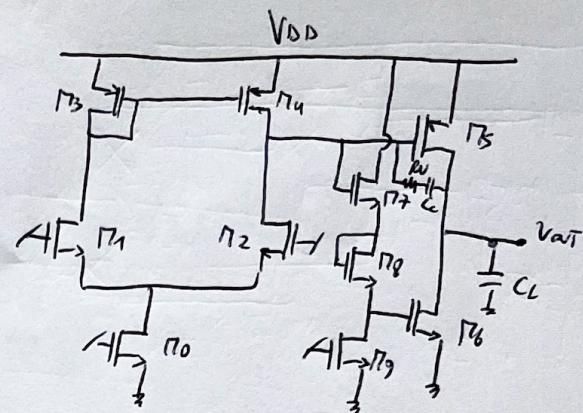In this way M_6 reacts in order to reduce its count only when needed, so we do not exceed static power consumption!




NOTE: the gain changes

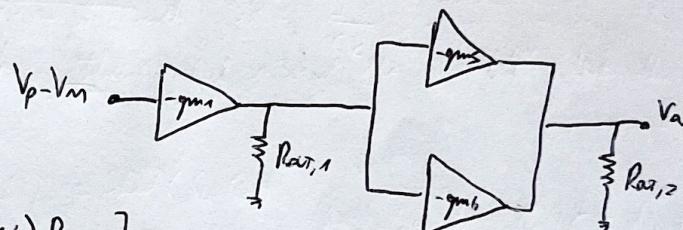

$$G_d = \frac{[g_{m1} \cdot R_{out,1}] \cdot [(g_{m2} + g_{m3}) R_{out,2}]}{G_2}$$

A possible alternative is the AC coupling:

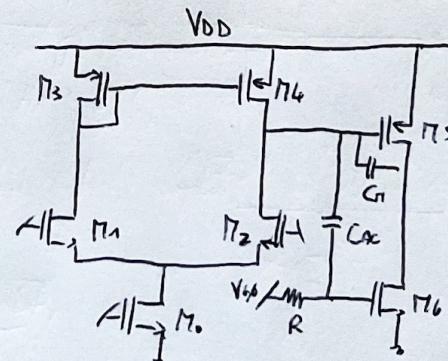the capacitance C_{ac} makes it possible to properly bias the M_6 transistor and also to let it come into action when needed.



FILTERS

→ Filter synthesis procedure:

- ① FILTER MASK
- ② FILTER TRANSFER FUNCTION
- ③ NETWORK IMPLEMENTATION (ideal)
- ④ NON-IDEALITIES OPTIMIZATION

→ Filters are divided (classified) into

LOW PASS; HIGH PASS; BAND PASS; STOP-BAND; EQUALIZERS (all pass)

The ideal filter should have

- 1) constant magnitude
- 2) linear phase shift proportional to ω

↓
Def: Let's consider a rigid filter in the pass-band of a filter. It is affected by a phase propagation delay τ , so

$$x(t) \rightarrow \boxed{\text{FILTER}} \rightarrow y(t) = Ax(t - \tau)$$

τ must affect only harmonic component, so each harmonic suffers from a $\Delta\phi = -\frac{2\pi}{T} \cdot \tau = -\omega\tau$ shift

These conditions however cannot be fulfilled by a real filter, since

Def: Let's consider an ideal LP on a linear frequency axis, so a rectangle. The inverse Fourier transform is a

$$\begin{aligned} h(t) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} H(\omega) e^{j\omega t} d\omega = \frac{H_0}{2\pi j\omega} \left[\frac{e^{j\omega t}}{j\omega} \right]_{-\infty}^{\infty} = \frac{H_0}{\pi t} \min(\omega t) \\ &\downarrow \\ &= \frac{\omega c H_0}{\pi} \frac{\min(\omega t)}{\omega t} = h_0 \cdot \min(\omega t) \end{aligned}$$

$h(t) \neq 0$ for $t < 0 \Rightarrow$ ANTI-CAUSAL, NOT FEASIBLE!

→ Important definitions for the FILTER MASK are

A_{sp} ATTENUATION IN BAND-PASS (maximum)

A_{sb} ATTENUATION IN STOP-BAND (minimum)

ω_{cp} CUT-OFF FREQUENCY

ω_{sb} LOWER LIMIT OF THE STOP-BAND

$\omega_c = \sqrt{\omega_{bp} \cdot \omega_{ap}}$ GENERAL FREQUENCY OF A BAND-PASS FILTER

$Q = \frac{\omega_c}{\Delta\omega}$ Q FACTOR OF A BAND-PASS FILTER

(49)

$$K = \frac{W_{BP}}{W_{SB}} < 1 \quad \text{SECURITY INDEX} \quad (\text{lower} = \text{worse})$$

$$\epsilon_{BP} = \sqrt{10^{\frac{A_{BP}}{20}} - 1} \quad \text{MAXIMUM ATTENUATION INDEX IN BAND-PASS}$$

$$\epsilon_{SB} = \sqrt{10^{\frac{A_{SB}}{20}} - 1} \quad \text{MINIMUM ATTENUATION INDEX IN STOP-BAND}$$

$$K_E = \frac{\epsilon_{BP}}{\epsilon_{SB}} < 1 \quad \text{DISCRETINATON INDEX} \quad (\text{lower} = \text{better})$$

$$Z_{GD} = -\frac{d\phi}{dw} \quad \text{GROUP DELAY (ideally constant)}$$

ALL POLES FUNCTIONS

- BUTTERWORTH

They require maximum band-pass and stop-band flatness

$$\left. \frac{d^n}{dw^n} |H(jw)|^2 \right|_{w=0} = 0 \quad \text{for } n=1, 2, \dots, 2n-1$$

$$\left. \frac{d^n}{dw^n} |H(jw)|^2 \right|_{w=\infty} = 0 \quad \text{for } n=1, 2, \dots, 2n-1$$

For a required $\omega_0 = 1 \text{ rad/s}$ angular frequency, these conditions are fulfilled by

$$|H(jw)|^2 = \frac{1}{1 + w^{2n}}$$

All poles are placed on a circle of radius $\omega_0 = 1 \text{ rad/s}$ on the complex plane, while

$$Q = \frac{1}{2\zeta} = \frac{|P|}{2\operatorname{Re}[P]} = \frac{1}{2} \quad \text{if REAL}$$

Poles are equally spaced and form the next on the circle by $\frac{\pi}{m}$ and the ones with half Q factors are $\frac{\pi}{2n}$ from from the m th order.

In order to achieve a lower A_{BP} than 3dB we may choose a different ω_0 , then having

$$|H(jw)|^2 = \frac{1}{1 + \left(\frac{w}{\omega_0}\right)^{2n}}$$

Let's fulfill the yes:

$$\frac{1}{1 + \left(\frac{\omega_{BP}}{\omega_0}\right)^{2n}} \geq \frac{1}{1 + \epsilon_{BP}^2} \Rightarrow \omega_0 \geq \frac{\omega_{BP}}{\epsilon_{BP}^{1/n}}$$

$$\frac{1}{1 + \left(\frac{\omega_{SB}}{\omega_0}\right)^{2n}} \leq \frac{1}{1 + \epsilon_{SB}^2} \Rightarrow \omega_0 \leq \frac{\omega_{SB}}{\epsilon_{SB}^{1/n}}$$

(50)

DEM: $\omega_0 \geq \frac{\omega_{BP}}{E_B^{1/m}}$ & $\omega_0 \leq \frac{\omega_{SB}}{E_S^{1/m}}$, by multiplying the
first two from $E_S^{1/m}$ we get

$$\frac{\omega_{BP}}{E_B^{1/m}} \cdot E_S^{1/m} \leq \omega_0 E_S^{1/m} \leq \omega_{SB}$$



$$\omega_{BP} \cdot \kappa^{-1/m} \leq \omega_{SB}$$



$$\kappa^{-1/m} \leq \kappa^{-1}$$



$$\frac{1}{m} \ln(\kappa^{-1}) \leq \ln(\kappa^{-1})$$



$$M \geq \frac{\ln(\kappa^{-1})}{\ln(\kappa^{-1})}$$

And $\frac{\omega_{BP}}{E_B^{1/m}} \leq \omega_0 \leq \frac{\omega_{SB}}{E_S^{1/m}}$

BESSEL

They realize the maximum phase linearity,

$$\left. \frac{d^k \omega_0}{d \omega^k} \right|_{\omega=0} = 0 \quad \text{for } k=1, 2, \dots, M$$

They have poles placed outside the ω_0 characteristic frequency circle, in order to reach a better group delay, thus also a lower selectivity.

In order to realize this, we can either resort to $\omega_0 = 1 \text{ rad/s}$ and we try to see if a specific ω_0 will fulfill the requirement.

CHEBYSHEV - I

They realize the maximum selectivity, but with an in-band ripples.

$$\max \left\{ 1 - |H(j\omega)|^2 \right\}_{\omega \leq 1} \leq E_B^2 \quad \text{maximum ripple requirement}$$

$$\left. \frac{d^k |H(j\omega)|^2}{d\omega^k} \right|_{\omega \rightarrow \infty} = 0 \quad \text{for } k=1, 2, \dots, 2n-1 \quad \text{stop-band flatness}$$

The DC value must be set to 1 for ^{odd} order T.F. and to

$\frac{1}{\sqrt{1+E_B^2}}$ for even order T.F., in order to have $|H(j\omega)| \leq 1$ in band.

51

USEFUL CHEBYSHEV FORMULAS

$$m \geq \frac{\operatorname{arcln}(4\epsilon^{-1})}{\operatorname{arcln}(4\eta^{-1})}$$

$$\Gamma = \left(\frac{1 + \sqrt{1 + \epsilon_{bp}^2}}{\epsilon_{bp}} \right)^{1/m}$$

$$z_n = - \sin \left[(2n-1) \frac{\pi}{2m} \right] \frac{\Gamma^2 - 1}{2\Gamma} + j \cos \left[(2n-1) \frac{\pi}{2m} \right] \frac{\Gamma^2 + 1}{2\Gamma}$$

(for $n = 1, \dots, m$)

$m = \#$ of half oscillations in low-pass

Conside only ~~below~~ the one with $\prod_{k=1}^m [] < 0$

→ POLES AND ZEROS

• CHEBYSHEV II

They have imaginary conjugate zeros in stop band only to be a couple the real will HF disturbances.

$$\max \left\{ 1 - |H(j\omega)|^2 \right\}_{\omega \geq 1} \geq \epsilon_{SB}^2 \quad \text{minimum attenuation in stop band } (\epsilon = \frac{1}{\epsilon_{SB}})$$

$$\left. \frac{d^n}{d\omega^n} |H(j\omega)|^2 \right|_{\omega=0} = 0 \quad \text{for } n = 1, 2, \dots, 2m-1$$

• CHEB

They are a couple ripples both in stop band and in low-pass. Once n and the in-band ripples are set, the stop-band ripple is determined.

• GENERALIZED ELLIPTICAL

They give an additional degree of freedom, so we can independently set η and both ripples, but we get a bad E_{DD} .

→ ADDITIONAL DEMONSTRATION

It can be shown that for a Chebyshev-type-I filter it is

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 C_m^2(\omega)}$$

$\epsilon \triangleq$ ROLL-OFF FACTOR
 $C_m =$ Chebyshev polynomial

when

$$C_m(\omega) = \begin{cases} \cos \left[m \operatorname{arccos} \left(\frac{\omega}{\omega_{bp}} \right) \right] & \left(\frac{\omega}{\omega_{bp}} \leq 1 \right) \\ \operatorname{ch} \left[m \operatorname{sech} \left(\frac{\omega}{\omega_{bp}} \right) \right] & \left(\frac{\omega}{\omega_{bp}} \geq 1 \right) \end{cases} \quad (=1 \text{ for } \omega = \omega_{bp})$$

so

$$|H(j\omega_{bp})|^2 = \frac{1}{1 + \epsilon^2} \Rightarrow \epsilon = \sqrt{10 \frac{\omega_{bp}}{\omega_0} - 1} = \epsilon_{bp}$$

In order to derive $m = \frac{\operatorname{SetCh}(\eta \epsilon^{-1})}{\operatorname{SetCh}(\eta^{-1})}$ with $|H(j\omega_{bp})|^2 = \frac{1}{1 + \epsilon_{bp}^2 C_m^2(\omega_{bp})} \dots$

NORMALIZATION AND TRANSFORMATION

Filter synthesis is performed in a domain or referred to a low pass filter with $\omega_{\text{bp}} = 1 \text{ rad/s}$. Therefore we need normalize the transformation.

→ LOW PASS

$$\omega = \frac{\omega}{\omega_{\text{bp}}} \quad \text{in order to get } \omega_{\text{bp}} = 1 \text{ rad/s}$$

Starting from the normalized Butterworth polynomials subject to $\omega_0 = 1 \text{ rad/s}$ we need first to set

$$\hat{s} = \omega_{\text{bp}} s$$

s normalized low-pass with $\omega_0 = 1 \text{ rad/s}$

$$\hat{s} \quad " \quad " \quad " \quad " \quad " \quad \omega_0 \neq 1 \text{ rad/s}$$

Then, we get

$$s = \omega_{\text{bp}} \cdot \hat{s}$$

s low-pass

→ HIGH PASS

$$\omega = \frac{\omega_{\text{bp}}}{\omega} \quad \text{in order to have } \omega_{\text{bp}} = 1 \text{ rad/s and to flip the axis}$$

$$\hat{s} = \frac{\omega_{\text{bp}}}{s}$$

→ BAND-PASS

DEF: Let's consider the transformation

$$\hat{s} = \hat{p} + \frac{1}{\hat{p}}$$

↓


$$\hat{p}^2 - \hat{s}\hat{p} + 1 = 0$$

↓

$$\hat{p} = \frac{\hat{s} \pm \sqrt{\hat{s}^2 - 4}}{2} \Rightarrow \alpha + j\omega = \frac{\Lambda + j\omega \pm \sqrt{\Lambda^2 - \omega^2 + 2j\Lambda\omega - 4}}{2}$$

Now, the $\text{Im}[\cdot]$ axis of \hat{s} ($\Lambda = 0$) is mapped into
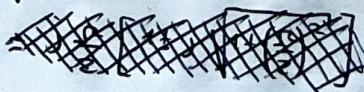
$$\alpha + j\omega = \frac{j\omega \pm j\sqrt{\omega^2 + 4}}{2} = j \frac{\omega}{2} \pm j \sqrt{1 + \left(\frac{\omega}{2}\right)^2}$$



as $\omega = 0$ and the $\text{Im}[\cdot]$ axis of \hat{s} is mapped into the points on the $\text{Im}[\cdot]$ axis of \hat{p} .

(53)

In particular,

$$\omega = 0 \Rightarrow \omega_{1,2} = \pm 1$$

$$\omega = 1 \Rightarrow \omega_{1,2} = +1,62; -0,62$$

Being $\omega_1 = 1$ the cut-off of the low pass filter, this is mapped into $s_{\text{cpl}} = 1$.
 Now if the low pass has a BW from 0 to 1, then it maps the BW from 0 to ω_0 to 0 to 1. So, to have a BW really s_{cpl} of the band pass, we need to map the BW from 0 to ω_0 to $s_{\text{cpl}} = \frac{1}{Q}$. Finally, to shift the center frequency, we shall replace \hat{p} , the freq $s = \hat{p} \cdot \omega_0$

↓

$$\hat{s} = Q \tilde{s} = Q \left[\hat{p} + \frac{1}{\hat{p}} \right] = Q \left[\frac{s}{\omega_0} + \frac{\omega_0}{s} \right] = Q \left[\frac{s^2 + \omega_0^2}{s \omega_0} \right]$$



which in terms of related frequency they converge to

$$\omega = Q \left(\frac{\omega^2 - \omega_0^2}{\omega \omega_0} \right)$$


ACTIVE CELLS

We can always split the T.F. in the product of 1st and 2nd order terms, so we can make each of them as a block and then cascade all of them (roughly decoupled) in order to make the full T.F.. We can use OPAMPS!

→ 1ST ORDER CELL

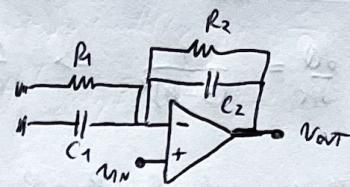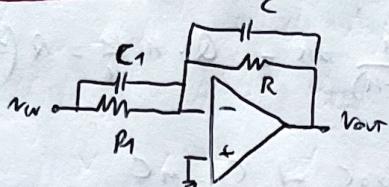

→ 2ND ORDER CELL (Sallen - Key)

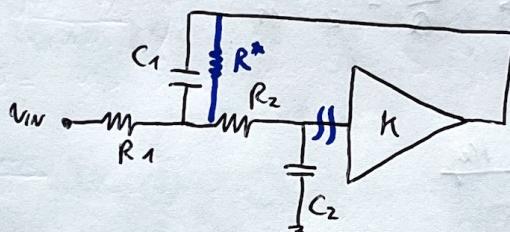

$$\Delta \text{loop}(s) = +K \cdot \frac{R_1}{R_1 + R^*}$$

$$a_1 = R^* C_1$$

$$b_1 = C_2 (R_2 + R_1 // R^*) + C_1 \cdot (R^* // R_1)$$

$$b_2 = C_1 C_2 (R^* // R_1) R_2$$

$$\Delta \text{loop}(s) = +K \cdot \frac{R_1}{R_1 + R^*} \cdot \frac{1 + \omega C_1 R^*}{1 + [C_2 (R_2 + R_1 // R^*) + C_1 (R^* // R_1)] + \omega C_1 C_2 R_2 (R^* // R_1)}$$

$$\downarrow R^* \rightarrow \infty$$

$$= +K \cdot \frac{\omega C_1 R_1}{\omega^2 C_1 C_2 R_1 R_2 + \omega [C_1 R_1 + C_2 (R_1 + R_2)] + 1}$$

By setting $\Delta \text{loop}(s) - 1 = 0$ we get the desired Lp term:

$$\omega^2 (R_1 R_2 C_1 C_2) + \omega [R_1 (1 - K) C_1 + (R_1 + R_2) C_2] + 1 = 0$$

$$\therefore \omega_0 = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}} \quad \text{and} \quad Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{C_1 R_1 + C_2 (R_1 + R_2) - K C_1 R_1}$$

$$\downarrow$$

$$= \frac{(R_1 C_1) \sqrt{R_1 R_2 C_1 C_2}}{(1 - K) + \frac{C_2}{R_1 C_1} (R_1 + R_2)} = \frac{\sqrt{\frac{R_2}{R_1} \frac{C_2}{C_1}}}{(1 - K) + \frac{C_2}{C_1} \left(1 + \frac{R_2}{R_1}\right)}$$

(55) Q signals are ratios \Rightarrow affected by sign changes, mitigated by mixing
 w/o signals are absolute values \Rightarrow affected by sign-to-sign changes

① $K \neq 1$ and $R_1 = R_2 = R$ and $C_1 = C_2 = C$

$$w_0 = \frac{1}{RC} \quad Q = \frac{1}{3-K} \quad \Rightarrow \quad n = 3 - \frac{1}{Q} \quad \text{dependent on } Q!$$


$$\frac{dQ}{dk} = \frac{1}{(3-n)^2} \quad \Rightarrow \quad \frac{dQ}{Q} = \frac{1}{(3-n)} \quad dk = Q \cdot n \frac{dn}{n} = Q \left(\frac{3-1}{Q} \right) \frac{dn}{n}$$

② $n=1$ and $R_1 = R_2 = R$ and $C_2 = C$ and $C_1 = nC$

$$w_0 = \frac{1}{\sqrt{n} RC} \quad Q = \frac{\sqrt{n}}{2} \quad \Rightarrow \quad n = 4Q^2$$

$$\frac{dQ}{dn} = \frac{1}{4\sqrt{n}} \quad \Rightarrow \quad \frac{dQ}{Q} = \frac{1}{2} \frac{dn}{n}$$

\rightarrow HIGH-PASS Sallen-Key

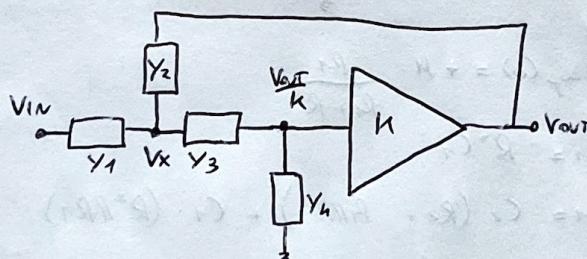

Def:

$$\begin{cases} (V_{IN} - V_x) Y_1 + (V_{out} - V_x) Y_2 = (V_x - \frac{V_{out}}{K}) Y_3 \\ V_x = \frac{V_{out}}{K} (1 + \frac{Y_4}{Y_3}) \end{cases}$$



$$V_{out} \left(Y_2 + \frac{Y_3}{K} \right) - V_x \left[Y_1 + Y_2 + Y_3 \right] = - V_{IN} Y_1$$



$$V_{out} \left(Y_2 + \frac{Y_3}{K} \right) - \frac{V_{out}}{K} \left[1 + \frac{Y_4}{Y_3} \right] \left[Y_1 + Y_2 + Y_3 \right] = - V_{IN} Y_1$$



$$V_{out} \left[Y_2 + \frac{Y_3}{K} - \frac{Y_1}{K} - \frac{Y_2}{K} - \frac{Y_3}{K} - \frac{Y_1 Y_4}{K Y_3} - \frac{Y_2 Y_4}{K Y_3} - \frac{Y_4}{K} \right] = - V_{IN} Y_1$$



$$\frac{V_{out}}{V_{IN}} = \frac{Y_1}{\frac{1}{K} \left[Y_1 + Y_2 + Y_3 + \frac{Y_1 Y_4}{Y_3} + \frac{Y_2 Y_4}{Y_3} + Y_4 - K Y_2 \right]} = \frac{K Y_1 Y_3}{Y_4 \left[Y_1 + Y_2 + Y_3 \right] + Y_1 Y_3 + Y_2 Y_3 (1 - K)}$$

→ UNIVERSAL CELL

Also called Koenig - Buelmann - Neumark (KBN)

DEF: let's consider a high-pass T.F.

$$\frac{V_{HP}(s)}{V_N} = \frac{\gamma s^2}{(s^2 + \frac{s w_0}{Q} + \frac{w_0^2}{\gamma^2})}$$


In order to let the integrator appear, let's divide for the highest power of s :

$$V_{HP} \left[1 + \frac{w_0}{Qs} + \frac{w_0^2}{s^2} \right] = \gamma V_N$$

↓

$$V_{HP} = \gamma V_N - \frac{w_0}{s} \frac{V_{HP}}{Q} - \frac{w_0^2}{s^2} V_{HP}$$

BLOCK DIAGRAM:

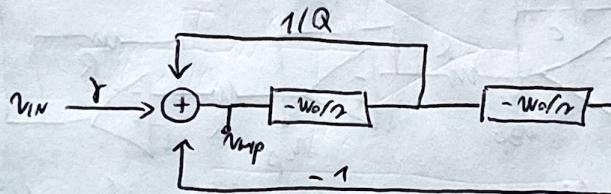


After the first integrator we get a BAND-PASS

$$\frac{V_{BP}(s)}{V_N(s)} = - \frac{\gamma w_0 s}{(s^2 + \frac{s w_0}{Q} + \frac{w_0^2}{\gamma^2})}$$

and after the next we get a LOW-PASS
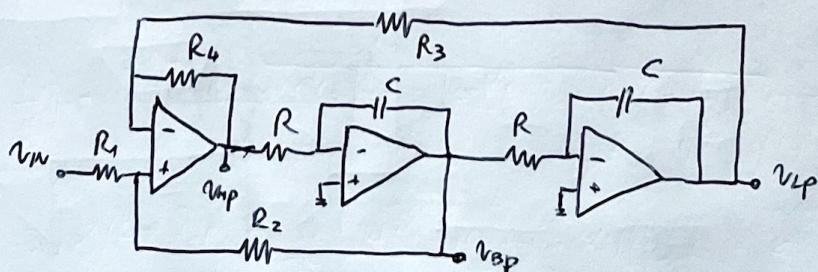
$$\frac{V_{LP}(s)}{V_N(s)} = \frac{\gamma w_0 s^2}{(s^2 + \frac{s w_0}{Q} + \frac{w_0^2}{\gamma^2})}$$





$$\Rightarrow V_{HP}(s) = \frac{R_2}{R_1 + R_2} \cdot \frac{R_3 + R_4}{R_3} \cdot V_N(s) + \frac{R_1}{R_1 + R_2} \cdot \frac{R_3 + R_4}{R_3} V_{BP}(s) + \left(-\frac{R_4}{R_3} \right) V_{LP}(s)$$

So we get

$$R_4 = R_3 \quad (\text{---} -1) \quad \gamma = \frac{2R_2}{R_1 + R_2} \quad \text{and} \quad \frac{1}{Q} = \frac{2R_1}{R_1 + R_2}$$

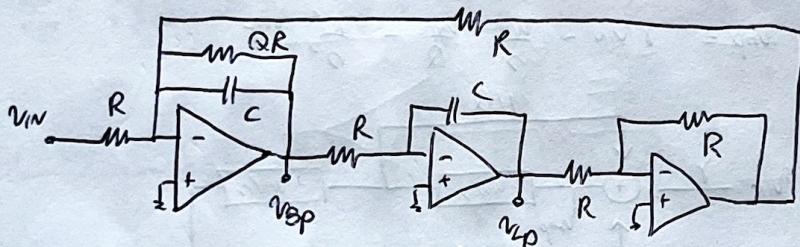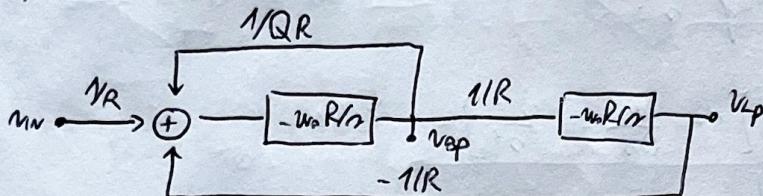(57) $\frac{B_1}{R_1} = 2Q - 1$ and $\lambda = \left(2 - \frac{1}{Q}\right)$ dependent of each other!
 If we sum the three digits in a word and we may get a T.F. with the zeros.

→ Tor-Tomas Am FLEISCHER-THOMAS
 We may sum just signs instead of numbers by using an integrator V.C.. To this aim we need to divide besides ~~the~~ entry the integrator by $\frac{1}{R}$ and to multiply integrator T.F. by R.




In a fully differential mode we don't need the resistors, it's enough to flip the cables.

By using with m_0 in all three V.C. we get a Fleischer-Thom. all with also the zeros.

The idea is to exploit interactions between different components in the same cell in order to compensate nonidealities. In active cells instead, each cell contributes independently to mobility.

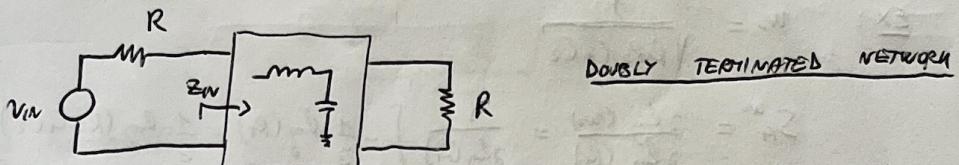DEM: These networks are PASSIVE COMPONENTS, like this:



At the maximum of the T.F. $Z_N = R$. At the mid frequency or the powers delivered to the load can be written as

$$P_L = \frac{\frac{V_{IN}^2}{2}}{R} = \frac{V_{IN}^2}{2R} |T(j\omega, X_0)|^2 \quad X_0 \text{ is mid value for } L \text{ and } C$$

Let's assume to have a maximum Ω at $\omega = \omega^*$, then

$$\left. \frac{\partial P_L}{\partial \omega} \right|_{\omega=\omega^*} = \frac{V_{IN}^2}{2R} \cdot 2 |T(j\omega, X_0)| \cdot \frac{\partial |T(j\omega, X_0)|}{\partial \omega} \Big|_{\omega=\omega^*} = 0$$

$$\left. \frac{\partial}{\partial \omega} |T(j\omega, X_0)| \right|_{\omega=\omega^*} = 0 = \left. \frac{\partial}{\partial X} |T(j\omega^*, X)| \right|_{X=X_0} \text{ by an absolute maximum}$$


So the reactivity of the T.F. to variations of L and C is nil at the powers and varies nil around it due to symmetry (ORCHARD THEOREM)

How to implement reactivities?


→ CREATORS

They are active shunts to provide an inductive impedance

(1)

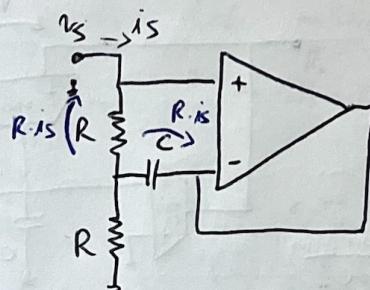

\Leftrightarrow

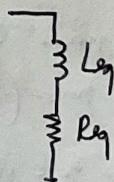

$$V_S = R \cdot i_S + (i_S + R.i_S \cdot C) \cdot R$$

$$\downarrow \\ = i_S [2R + sCR^2]$$

29 OCT 2024

SENSITIVITY ANALYSIS

$$S_x^Y = \frac{\frac{\partial Y}{\partial x}}{Y} = \frac{\partial \log(Y)}{\partial \log(x)}$$

$x = \text{unit parameter}$
 $y = \text{filter parameter}$
 $\log = \text{natural log ln}$

Ex: $N_D = \frac{1}{R_1 R_2 C_1 C_2}$

$$S_{N_D}^{W_0} = \frac{\partial \log(N_D)}{\partial \log(R_1)} = \frac{\partial \log(N_D)}{\partial \log(R_1)} \left[-\frac{1}{2} \log(R_1) - \frac{1}{2} \log(R_2 C_1 C_2) \right] = -\frac{1}{2}$$

same for $S_{R_2}^{W_0}$, $S_{C_1}^{W_0}$, $S_{C_2}^{W_0}$, and for $S_K^{W_0} = 0$

Ex: $Q = \frac{1}{[R_1(1-k)C_1 + (R_1+R_2)C_2] W_0}$

$$\begin{aligned} S_Q^{W_0} &= \frac{\partial}{\partial \log(R_1)} \left[-\log(W_0) - \log(R_1(1-k)(1 + (R_1+R_2)C_2)) \right] = \\ &= \frac{1}{2} - \frac{R_1}{2R_1} \left[\log(R_1(1-k)(1 + (R_1+R_2)C_2)) \right] = \\ &= \frac{1}{2} - R_1 \frac{(1-k)(C_1 + C_2)}{R_1(1-k)(1 + (R_1+R_2)C_2)} = \\ &= \frac{R_1[1-k](C_1 + (R_1+R_2)C_2) - 2C_1R_1(1-k) - 2C_2R_1}{2[R_1(1-k)(1 + (R_1+R_2)C_2)]} = \\ &= -\frac{C_1R_1(1-k) + (R_1 - R_2)C_2}{2[R_1(1-k)(1 + (R_1+R_2)C_2)]} \end{aligned}$$

The others can be found similarly in the same way...

MISMATCH ISSUE IN GYRATORS

If the two gm_2 transconductances do not match, we have that

$$gm_2' = gm_2 + \frac{\Delta gm}{2}$$

$$gm_2'' = gm_2 + \left(-\frac{\Delta gm}{2}\right)$$



$$i_{IN} = gm_2' v_c = \frac{v_s gm_1 gm_2'}{2C} + \frac{(v_s gm_1 \Delta gm)}{2\omega C}$$

$$i_{OUT} = gm_2'' v_c = \frac{v_s gm_1 gm_2}{2C} - \frac{(v_s gm_1 \Delta gm)}{2\omega C}$$

$$i_{IN} - i_{OUT} = \Delta i = \frac{v_s gm_1}{2C} \cdot \frac{\Delta gm}{gm_2} gm_2 = i_s \frac{\Delta gm}{gm_2} = \frac{v_s}{2Lg} \frac{\Delta gm}{gm_2}$$


We basically get the return:
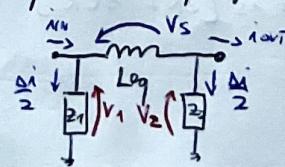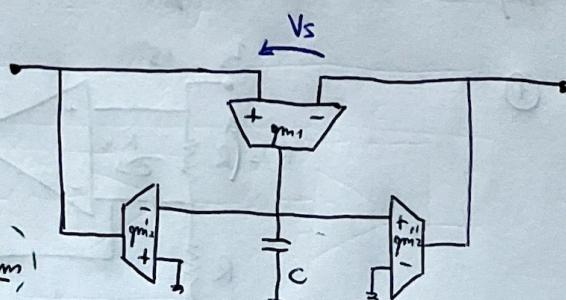
$$z_2 = \frac{v_2}{\frac{\Delta i}{2}} ; z_1 = \frac{v_1}{\frac{\Delta i}{2}}$$



$$\begin{cases} v_1 = \frac{v_s}{2} + v_{in} \\ v_2 = -\frac{v_s}{2} + v_{out} \end{cases}$$

② Antenna Circuit


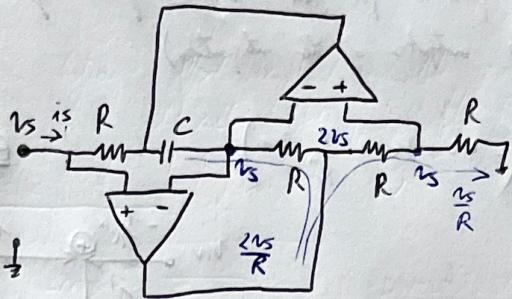


$$\frac{2V_s}{R} \cdot \frac{1}{2C} = i_s \cdot R$$

↓

$$\frac{2V_s}{i_s} = \approx CR^2$$

③ Other solutions

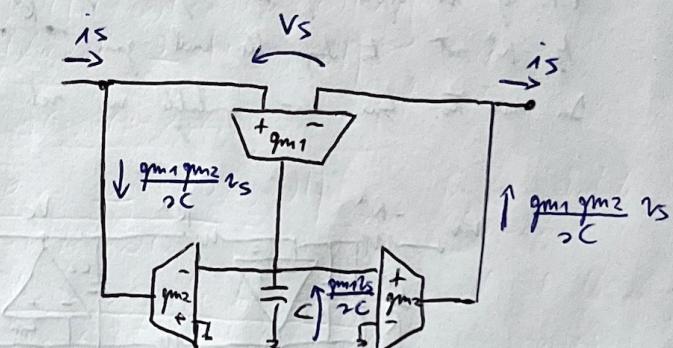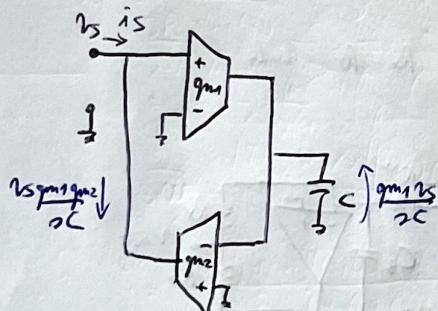

Problems of generators are

- limited GSWP of active shorts
- noise


→ INTEGRATORS (DEVI.)

Let's consider this 3rd order ladder network:

$$\text{KVL: } v_{in} - v_c = (sL_1 + R)i_1$$

$$\text{KVL: } v_c - v_{out} = sL_2 i_2$$

$$\text{KCL: } i_1 - i_2 = sC v_c$$

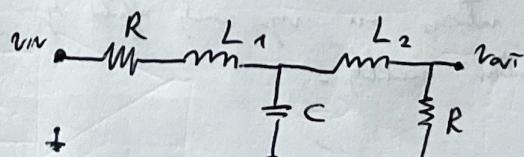

Find the voltage
(inductor anti, capacitor voltage)

Now write the anti as auxiliary voltage divided by an auxiliary resistance R'

$$\left\{ \begin{array}{l} v_{in} - v_c = \frac{sL_1 + R}{R'} \cdot v_1 \\ v_c - v_{out} = \frac{sL_2}{R'} v_2 \end{array} \right.$$

$$\frac{v_1 - v_2}{R'} = sC v_c$$

$$v_{aux} = \frac{R}{R'} v_2$$


(61) Now divide each equation for the highest power of s in order to let the integrators appear: (with the outputs of the integrators)

↓

$$v_1 = -\frac{R^a}{sL_1} \left(-v_{IN} + v_C + \frac{R^a}{R^a} v_1 \right)$$

Block Diagram

$$v_C = -\frac{1}{sCR^a} (-v_1 + v_2)$$

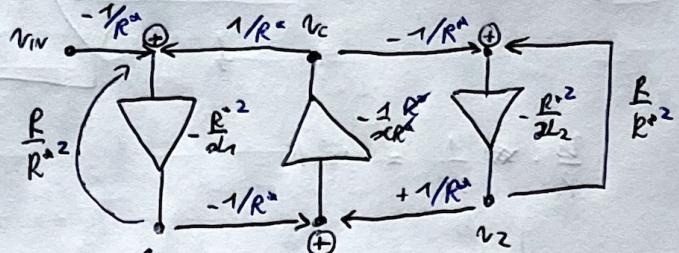


$$v_2 = -\frac{R^a}{sL_2} (-v_C + v_{out})$$

$$v_{out} = \frac{R^a}{R^a} v_2$$

We may use initial gains in order to remove signals, so we need to divide each T.F. of the inputs of the integrator by $\frac{1}{R^a}$ and then to multiply each integrator T.F. by R^a , not to change the overall gain.

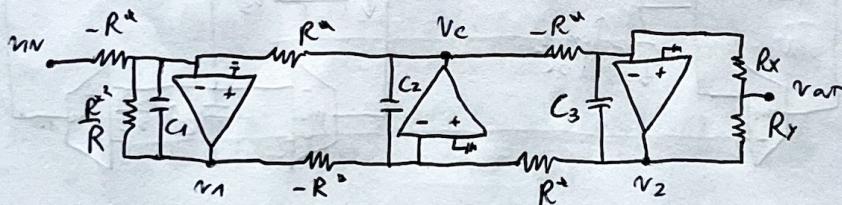In order to have v_{out} available we add an $R_x - R_y$ bridge



$$\left\{ R_x + R_y = \frac{R^{a^2}}{R} \right.$$

$$\left. v_{out} = \frac{R_x}{R_x + R_y} v_2 = \frac{R}{R^a} v_2 \Rightarrow R_x = R^a \text{ and } R_y = \frac{R^{a^2}}{R} - R^a \right.$$

The resistors are very nearly affected by feedback capacitors' variability, but they are affected by resistor variability.

Noise And Op-Amp Non-Idealities

Dynamic Range \geq ratio between maximum and minimum signal levels handled by the circuit.

DEF: Let's consider this circuit

The maximum output signal is $2V_{DD}$, so a sinusoid with $V_{PEAK} = \frac{2V_{DD}}{2}$, so $\langle V_{out}^2 \rangle = \frac{d^2 V_{DD}^2}{8}$

While the RMS value of the sinusoid due to just the resistor R is

$$uNTR \cdot \frac{1}{4RC} = \frac{uT}{C}$$

and the additional noise due to the amplifier is $F \cdot \frac{uT}{C}$, so we get

$$DR = \sqrt{\frac{2^2 V_{DD}^2 / 8}{(1+F) uT / C}} = 2V_{DD} \sqrt{\frac{C}{8uT(1+F)}}$$

So, to measure the DR (which means to measure the number of bits of an A/D converter, being $DR = \frac{FSR}{LSB}$) we need to measure both C (more one) and V_{DD}

(more power dissipation)

On each ~~full~~ half-period the capacitor is charged up to $2V_{DD}$ and then discharged, so it dissipates

$$\frac{2V_{DD} \cdot C \cdot V_{DD}}{T} \cdot \frac{\Delta Q}{\Delta t}$$



Noise

Let's consider this amplifier

$$\textcircled{1} \quad \text{error}_1 = L_1 \cdot \frac{R}{R_1} \cdot \frac{1}{4\pi f_0 R C}$$


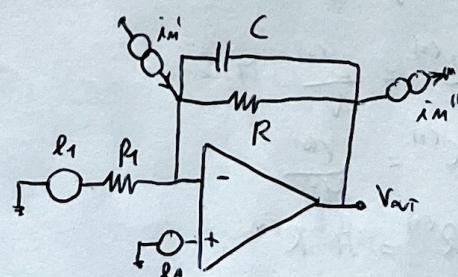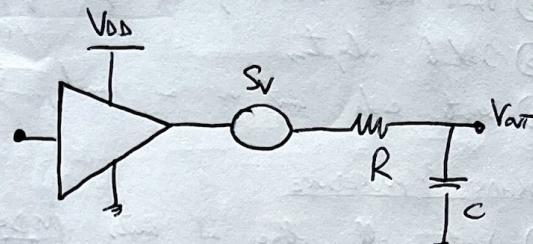
$$S_{V_{out}, M} = S_{V_{in}, M} \left(\frac{R}{R_1} \right)^2 \frac{1}{4RC} = \frac{uT}{C} \frac{R}{R_1}$$



$$\textcircled{2} \quad V_{out,2} \Rightarrow S_{I,R2} \cdot R^2 \cdot \frac{1}{4RC} = \frac{hT}{C}$$

$$\textcircled{3} \quad V_{out,A} \Rightarrow S_A \cdot \frac{w_0}{4} + S_A \left(1 + \frac{R}{R_1}\right)^2 \frac{w_0}{4}$$

we take two into account due to the finite GBWP of the amplifier, so that we consider the HF transfer to be limited by the ENBW = $\frac{w_0}{4}$

To be more accurate we should consider that the finite comp. of the amplifier affects the small T.F., i.e.

$$L_{out,A} = L_A \left[1 + \frac{R}{R_1} \frac{1}{1 + \omega RC} \right] \cdot \frac{1}{\left(1 + \frac{\omega}{w_0}\right)} = L_A \left(1 + \frac{R}{R_1}\right) \frac{\left(1 + \frac{\omega}{w_0}\right)}{\left(1 + \frac{\omega}{w_0}\right)\left(1 + \frac{\omega}{w_0}\right)}$$

$$w_0 \text{ freq} = \frac{1}{C(R_1/R)}$$

If we rewrite it in this way, we can use the standard integral

$$\int_0^{+\infty} \left| \frac{1 + \frac{\omega}{w_0}}{\frac{\omega^2}{w_0 w_M} + \omega \frac{(w_0 + w_M)}{w_0 w_M} + 1} \right|^2 d\omega = \frac{w_0 w_M}{(w_0 + w_M)} \frac{1}{h} \left[1 + \frac{w_0 w_M}{w_0^2} \right] = ENBW$$

$$\textcircled{3} \quad L_{out,A} = S_A \cdot \left(1 + \frac{R}{R_1}\right)^2 \cdot ENBW \xrightarrow{w_M \gg w_0} S_A \cdot \left(1 + \frac{R}{R_1}\right)^2 \cdot \frac{w_0}{4} \left[1 + \frac{w_0 w_M}{w_0^2} \right]$$

which converges to the approximated result. \downarrow
 $= S_A \left(1 + \frac{R}{R_1}\right)^2 \cdot \left[\frac{w_0}{4} + \frac{w_0}{4} \left(\frac{R_1}{R_1 + R_0} \right)^2 \right]$

$$\textcircled{4} \quad \text{Sout} = \underbrace{S_{V-IN} G^2}_{\text{INPUT}} \cdot \frac{w_0}{4} + hTR \cancel{\left(\frac{w_0}{4} + S_{V-A} \left[\gamma + (1+G)^2 \right] \frac{w_0}{4} + hTR G \frac{w_0}{4} \right)} \\ \downarrow \\ = S_{V-IN}^2 \frac{w_0}{4} \left[1 + \frac{hTR}{S_{V-IN}} \left(\frac{1+G}{G^2} \right) + \frac{S_{V-A}}{S_{V-IN}} \frac{\gamma + (1+G)^2}{G^2} \right] = S_{V-IN} \cdot G^2 \frac{w_0}{4} \left[1 + F \right]$$

So, in order to minimize F , we need to

- 1) have $G > 1$
- 2) resistor value noise is $< S_{V-IN}$
- 3) amplifier value noise is $< S_{V-IN}$
- 4) limit the bandwidth by a suitable GBWP

$$\begin{cases} G = \frac{R}{R_1} \\ \gamma = \frac{w_M}{w_0} \end{cases}$$

LADDER NETWORKS Summary

KTF-1971-1000 97A-90 and 20

2

→ KL PROCEDURE

- ① Use KL in order to write relations among STATE VARIABLES (i_L, v_C)
- ② Divide each number by the highest power of ω
- ③ Isolate integrators
- ④ Write each unit or an auxiliary voltage divided by R^a

→ FLOWCHART PROCEDURE

- ① Write all integrators and units INSIDE COMPONENTS
- ② Draw integrators
- ③ Use KL to write the inputs of integrators (i_L, v_C)
- ④ Divide the branches going into V.C. by R^a and multiply the integrators T.F. for R^a
- ⑤ Multiply units on the down side for R^a , divide branches going up for R^a and multiply branches going down for R^a
- ⑥ Multiply for (-) inputs of integrators and integrators T.F.

→ DE-NORMALIZATION

Remember $w_o \propto \frac{1}{\sqrt{LC}}$ and $Q \propto w_o RC$, so to shift us to a value N times higher we need to multiply

$$\begin{cases} L^{(1)} = \frac{L^{(0)}}{N} \\ C^{(1)} = \frac{C^{(0)}}{N} \end{cases}$$

This does not change Q .


Moreover, to further decrease C without changing w_o and Q we need to multiply L and R by M :

$$\begin{cases} L^{(1)} = \frac{L^{(0)}}{N} \cdot M \\ C^{(1)} = \frac{C^{(0)}}{MN} \\ R^{(1)} = M \cdot R^{(0)} \end{cases}$$

OP - AMP Non IDEALITIES

Let's consider an integrator:

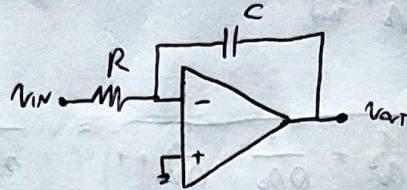We know that the forward gain is the opAMP, while the $\beta(s)$ is



$$\beta(s) = \frac{R}{R + \frac{1}{sC}} = \frac{sCR}{1 + sCR}$$

$$\begin{cases} CR = \omega_0 \\ \frac{1}{CR} = \omega_0 \end{cases}$$

$$\frac{1}{\beta}(s) = \frac{1 + \frac{s}{\omega_0}}{\frac{s}{\omega_0}} = 1 + \frac{\omega_0}{s}$$

The loop gain is equal to $|loop(s)| = -\frac{A_0}{(1+s\tau)} \frac{s\omega_0}{(1+s\omega_0)}$, it has a low frequency pole due to the opAMP, a zero in DC and a pole at ω_0 , so the loop gain @ middle freq is

$$|loop(MF)| = A_0 \frac{\omega_0}{\tau} = \frac{GBWP}{f_0} \quad (\text{we need } GBWP \geq 100 \text{ fo to have a flat loop gain})$$

and the closed loop transfer function has a pole at

$$\omega_L = \frac{\omega_0}{A_0} = \frac{1}{A_0 RC} \quad (\text{MILLER POLE})$$

and another pole at

$$\omega_H = GBWP$$

So, in the end,

$$H_{int}(s) = \frac{-A_0}{(1 + \frac{s}{\omega_L})(1 + \frac{s}{\omega_H})}$$

DC GAIN		
LOW FREQUENCY		POLE
HIGH FREQUENCY	POLE	

DC GAIN AND LF POLE EFFECT

$$T(s) = \frac{\omega_0^2 \cdot \frac{1}{s^2}}{\left(\omega_0^2 + \frac{\omega_0}{Q} + \frac{1}{s^2}\right)} = \frac{\left(\frac{-\omega_0}{s}\right)^2}{\left(-\frac{\omega_0}{s}\right)^2 - \frac{1}{Q} \left(\frac{\omega_0}{s}\right) + 1} = \frac{H_{int}^2(s)}{H_{int}^2(s) - \frac{1}{Q} H_{int}(s) + 1}$$

Let's consider now $H_{int}(s) = \frac{-A_0}{1 + \frac{s}{\omega_L}}$ at low frequency, we can write it as

$$H_{int}(s) = -\frac{1}{\left(\frac{1}{A_0} + \frac{s}{\omega_0}\right)}$$

and replace it into $T(s)$

(66)

$$\begin{aligned}
 T(s) &= \frac{\frac{1}{(\frac{1}{A_0} + \frac{2}{\omega_0})^2}}{\frac{1}{(\frac{1}{A_0} + \frac{2}{\omega_0})^2} + \frac{1}{Q(\frac{1}{A_0} + \frac{2}{\omega_0})} + 1} = \frac{1}{1 + \frac{1}{Q} \left(\frac{1}{A_0} + \frac{2}{\omega_0} \right) + \left(\frac{1}{A_0} + \frac{2}{\omega_0} \right)^2} \\
 &\downarrow \\
 &= \frac{1}{\frac{\omega^2}{\omega_0^2} + \frac{2\omega}{\omega_0 A_0} + \frac{1}{A_0^2} + \frac{1}{Q A_0} + \frac{2}{Q \omega_0} + 1} = \frac{\omega_0^2}{\omega^2 + \frac{2\omega \omega_0}{A_0} + \frac{\omega_0^2}{A_0^2} + \frac{\omega_0^2}{Q A_0} + \omega_0^2 + \frac{2\omega_0}{Q}} \\
 &\downarrow \\
 &= \frac{\omega_0^2}{\omega^2 + \omega \omega_0 \left(\frac{1}{Q} + \frac{2}{A_0} \right) + \omega_0^2 \left(1 + \frac{1}{Q A_0} + \frac{1}{A_0^2} \right)}
 \end{aligned}$$

$$\Rightarrow \omega' = \omega_0 \sqrt{1 + \frac{1}{A_0 Q} + \frac{1}{A_0^2}} \quad \text{RADIAL FREQUENCY SHIFT}$$

$$\Rightarrow \frac{1}{Q'} \approx \left(\frac{1}{Q} + \frac{2}{A_0} \right) \rightarrow Q \left(\frac{1}{Q} - \frac{1}{Q'} \right) = \frac{Q' - Q}{Q' Q} \cdot Q = \frac{\Delta Q}{Q} = -\frac{2Q}{A_0} \quad \text{IN-BAND DROP}$$

→ FINITE CBWP EFFECT

Let's write now the real integrator T.F. at high frequency:

$$H_{int}(s) = -\frac{\omega_0}{s^2} \frac{1}{\left(1 + \frac{2}{\omega_m}\right)^2}$$

so we get

$$\begin{aligned}
 T(s) &= \frac{\left(\frac{\omega_0}{s}\right)^2 \cdot \frac{1}{\left(1 + \frac{2}{\omega_m}\right)^2}}{\left(\frac{\omega_0}{s}\right)^2 \frac{1}{\left(1 + \frac{2}{\omega_m}\right)^2} + \frac{\omega_0}{Q s} \frac{1}{\left(1 + \frac{2}{\omega_m}\right)} + 1} \\
 &\downarrow \\
 &= \frac{1}{1 + \frac{\omega^2}{Q \omega_0} \left(1 + \frac{2}{\omega_m}\right) + \frac{2^2}{\omega_0^2} \left(1 + \frac{2}{\omega_m}\right)^2}.
 \end{aligned}$$

This T.F. has two complex conjugate poles + the additional pole due to the integrator. Omitting to write at $|s| \ll \omega_m$ we may write

$$\left(1 + \frac{2}{\omega_m}\right)^2 \left[\frac{2^2}{\omega_0^2} + \frac{2}{Q \omega_0 \left(1 + \frac{2}{\omega_m}\right)} + \frac{1}{\left(1 + 2/\omega_m\right)^2} \right] = 0$$

$$\left(1 + \frac{2}{\omega_m}\right)^2 \left[\frac{2^2}{\omega_0^2} + \frac{2}{Q \omega_0} \left(1 - \frac{2}{\omega_m}\right) + \left(1 - \frac{2}{\omega_m}\right)^2 \right] = 0$$

so we get

$$\frac{w_0^2}{Q w_m} \left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right] + \frac{2}{w_0} \left(\frac{1}{Q} - 2 \frac{w_0}{w_m} \right) + 1 = 0$$

↓

$$\frac{w^2}{Q^2} + 2 \frac{w_0}{\left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right]} \frac{\left(1 - 2 \frac{w_0}{w_m} Q \right)}{Q} + \frac{w_0^2}{\left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right]} = 0$$

$$\Rightarrow w_0' = \sqrt{1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2} \approx w_0 \left(1 + \frac{w_0}{2 Q w_m} \right) \quad (w_m \gg w_0)$$

$$\Rightarrow \frac{1}{Q'} \approx \frac{1}{Q} \frac{\left(1 - 2 \frac{w_0}{w_m} Q \right)}{\left[1 - \frac{w_0}{Q w_m} + \left(\frac{w_0}{w_m} \right)^2 \right]} \approx \left(\frac{1}{Q} - 2 \frac{w_0}{w_m} \right) \quad (w_m \gg w_0)$$

$$\text{So } \frac{Q' - Q}{Q'} \approx \frac{\Delta Q}{Q} = 2 \frac{w_0}{w_m} \cdot Q$$

Conclusion: the real response of the opAMP affects the w_0 and the Q of the real integrator, so mostly it affects the gain of the filter, which becomes more sensitive if the Q factor is higher! This happens because the $\frac{\Delta Q}{Q}$ term is proportional to Q .

Although the positive Q shifts due to HF influences may exceed the negative shift due to the DC gain and the LF pole, we consider the worst case, setting a constant on the maximum absolute value for both the positive and negative swing.

$$\left| \frac{\Delta Q}{Q} \right| \leq \text{Error \%}$$

As a final result, we may consider the contribution arising from the positive zero in the open loop Op-AMP T.F., or

$$H_{int}(s) = - \frac{w_0}{s} \left(1 - \frac{2}{w_2} \right)$$

$$T(s) = \frac{H_{int}(s)}{H_{int}^2(s) - \frac{1}{Q} H_{int}(s) + 1} = \frac{\left(\frac{w_0}{s} \right)^2 \left(1 - \frac{2}{w_2} \right)^2}{\left(\frac{w_0}{s} \right)^2 \left(1 - \frac{2}{w_2} \right)^2 + \frac{w_0}{Q s} \left(1 - \frac{2}{w_2} \right) + 1}$$

The poles will be given by the roots of

$$\frac{2}{w_0^2} + \frac{2}{Q w_0} \left(1 - \frac{2}{w_2} \right) + \left(1 - \frac{2}{w_2} \right)^2 = 0$$

(68)

So we get

$$\frac{\gamma^2}{\omega_0^2} \left[1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2 \right] + \left(\frac{2}{Q\omega_0} \left(1 - \frac{\omega_0}{\omega_2} \right)^2 \frac{\omega_0}{\omega_2} Q \right) + 1 = 0$$

$$\downarrow$$

$$\frac{\gamma^2 + \frac{2\omega_0}{\left[1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2 \right]}}{\frac{\left(1 - \frac{2\omega_0}{\omega_2} Q \right)}{Q}} + \frac{\omega_0^2}{\left[1 - \frac{\omega_0}{Q\omega_2} + \frac{\omega_0}{\omega_2} \right]^2} = 0$$

So


$$\omega_0' = \sqrt{1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2} \approx \omega_0 \left(1 + \frac{2\omega_0}{Q\omega_2} \right) \quad (\omega_2 \gg \omega_0)$$

$$\frac{1}{Q'} = \frac{1}{Q} \frac{\left(1 - \frac{2\omega_0}{\omega_2} Q \right)}{\sqrt{1 - \frac{\omega_0}{Q\omega_2} + \left(\frac{\omega_0}{\omega_2} \right)^2}} \approx \frac{1}{Q} \left(1 - \frac{2\omega_0}{\omega_2} \right) \quad (\omega_2 \gg \omega_0)$$

$$\downarrow$$

$$\left(\frac{1}{Q} - \frac{1}{Q'} \right) Q \approx \frac{\Delta Q}{Q} = \left(\frac{2\omega_0}{\omega_2} Q \right) \quad \text{POSITIVE SHIFT, line for the LSWP}$$

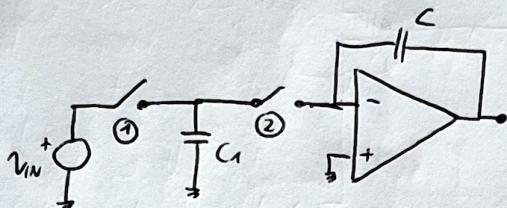In the low frequency range we'd require very large resistors in order to have suitable values of capacitors, but they are hard to be made in integrated technology, so we use switched capacitors.



Phase ① \Rightarrow ① is closed and C_1 stores $Q = C_1 \cdot V_{IN}$

Phase ② \Rightarrow ② is closed and C_1 charges C , $\Rightarrow v_C = \frac{C_1 V_{IN}}{C}$

At the output we get a staircase with slope $\frac{C_1 V_{IN}}{C \cdot T}$

The output of an integrator has a slope of

~~$\frac{V_{IN}}{RC}$~~

\Rightarrow we can say that the switched capacitor provides $R_{eq} = \frac{1}{C_1}$

- ADVANTAGES:
- much larger resistors by using null capacitors
 - no need of buffer output stages in ladder networks made of integrators
 - no dc drifts on the ratio between the capacitors, which can be controlled by null

DISADVANTAGES: we have to deal with a discrete signal, so Shanon must be respected

(A1)

ANALYSIS OF A GSCODE - COMPENSATED OTA

The following is an idea to compute a two-stage OTA in an Ohm-like technique but without using too much current.

Idea: substitute the current buffer with a cascade in the first stage.

The T.F. will have this general form:

$$T(s) = C(s) \cdot \frac{a_2 s^2 + a_1 s + 1}{b_3 s^3 + b_2 s^2 + b_1 s + 1}$$

because we have three independent capacitors and one of them is directly attached to the output node from ground.

We find that:

$$C(s) = g_{m1} R_{out,1} g_{m5} R_{out,2}$$

$$b_1 = C_1 R_1^{(0)} + C_2 R_2^{(0)} + C_C R_C^{(0)}$$

$$b_2 = C_1 C_2 R_1^{(0)} R_2^{(1)} + C_1 C_2 R_1^{(0)} R_C^{(1)} + C_2 C_C R_2^{(0)} R_C^{(2)}$$

$$b_3 = C_1 C_2 C_C R_1^{(0)} R_2^{(1)} R_C^{(1,2)}$$

so for the denominators we need

$$R_1^{(0)} = R_1$$

$$R_2^{(0)} = R_2$$

$$R_2^{(1)} = R_2$$

$$R_C^{(1)} = \frac{1}{g_{m3}} + R_2 \approx R_2$$

$$R_C^{(2)} = \frac{1}{g_{mB}}$$

in order to compute $R_C^{(0)}$ we may substitute C_C with a current generator i_s . This current will flow basically entirely through M_{B2} , thus generating:

$$V_{GS} = i_s R_1$$

so we get the following balance at the output node:

$$i_s + g_{m5} R_1 i_s + \frac{V_2}{R_2} = 0$$

$$V_2 = -i_s R_2 (1 + g_{m5} R_1)$$


Then we know that

$$V_1 \approx \frac{i_s}{g_{mB}}$$

so we get

$$V_S = V_1 - V_2 = \left(\frac{1}{g_{mB}} + R_2 + g_{m5} R_1 R_2 \right) i_s$$

MILLER EFFECT

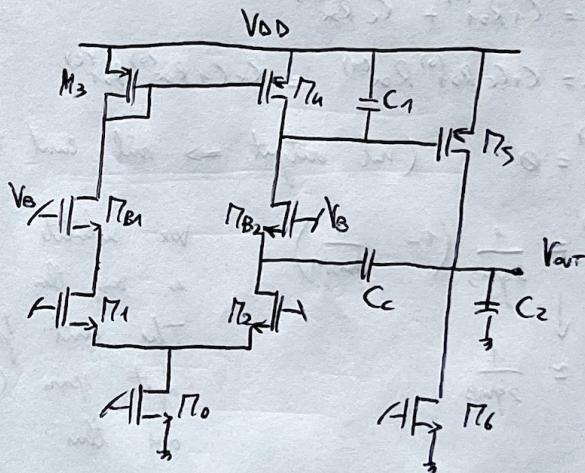

Therefore we get

$$R_C^{(o)} \approx g_{mS} R_1 R_2$$

and we can safely say that $b_1 \approx C_1 g_{mS} R_1 R_2$ at first instance. Then, we have that

$$b_2 = C_1 C_2 R_1 R_2 + C_1 C_c R_1 R_2 + C_2 C_c R_2 \cdot \frac{1}{g_{mB}} \approx C_1 R_1 R_2 (C_2 + C_c)$$

$$b_3 = C_1 C_2 C_c R_1 R_2 \frac{1}{g_{mB}}$$

Let's consider now the numerator of the T.F.

~~numerator~~

$$a_1 = C_1 R_{o1}^{(o)} + C_c R_{oc}^{(o)}$$

$$a_2 = C_1 C_c R_{o1}^{(o)} R_{oc}^{(1)} = C_c (C_1 R_{oc}^{(o)}) R_{o1}^{(c)}$$

$$R_{o1}^{(o)} = 0 \quad (\text{nil output} \Rightarrow \text{nil curr through } I_{S1} \Rightarrow \text{nil } v_{g,s} = v_s)$$

$$R_{oc}^{(o)} = \frac{1}{2g_{mS}} \left(1 - \frac{1}{g_{mS} R_1} \right)$$

$$\downarrow \\ \approx \frac{1}{2g_{mB}}$$

We substitute C_c with a curr source. If the output is v_s , then it flows into I_{S1} , so $v_{g,s} = -\frac{i_S}{g_{mS}}$. The curr from is merged with the one due to the input gain (splits), so we have $i_S - id$ through R_{B2} and thus

$$i_S - id - (id) = i_S - 2id$$

through R_1 . So we get

$$-\frac{i_S}{g_{mS} R_1} = i_S - 2id$$

↓

$$id = \frac{i_S}{2} \left[1 + \frac{1}{g_{mS} R_1} \right]$$

so the voltage at the node of R_{B2} will be


$$\frac{(i_S - id)}{g_{mB}} = \frac{1}{g_{mB}} \left[\frac{i_S}{2} - \frac{1}{g_{mS} R_1} \frac{i_S}{2} \right] = v_s$$

$$\Rightarrow \frac{v_s}{i_S} = \frac{1}{2g_{mB}} \left[1 - \frac{1}{g_{mS} R_1} \right]$$

Now, since $R_{o1}^{(o)} = 0$, it's better to use the second form, in order not to get indeterminate results:


$$id = i_S = -g_{mS} v_s$$

COMPUTATION OF $R_{o1}^{(c)}$

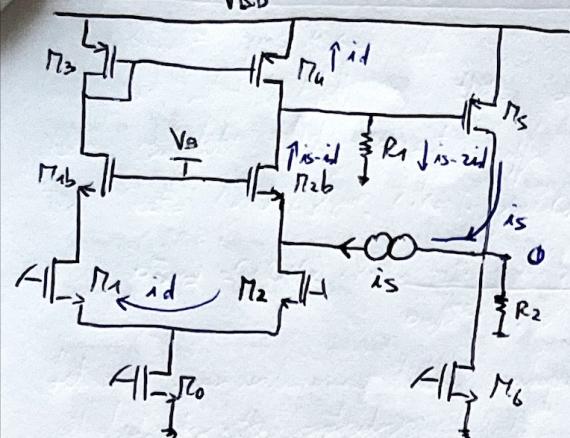

(A₃)

COMPUTATION OF $R_{o1}^{(c)}$

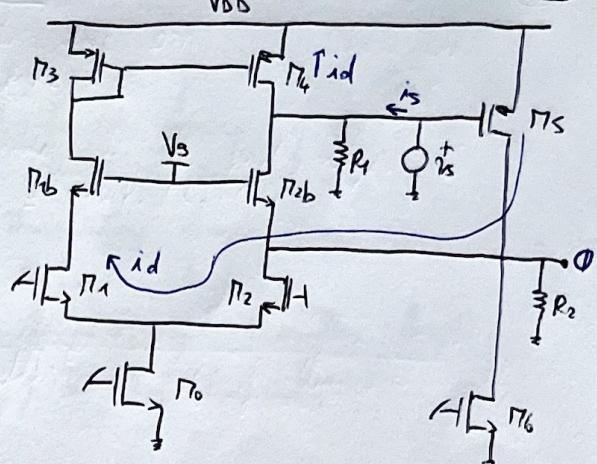

Then $i_s = id + \frac{v_s}{R_1} \approx id = -gm_s v_s$

so

$$R_{o1}^{(c)} \approx -\frac{1}{gm_s}$$

in the end we have

$$\alpha_1 \approx \frac{C_c}{2gm_B}$$

$$\alpha_2 = C_c C_1 \frac{1}{2gm_B} \left(-\frac{1}{gm_s} \right)$$

and

$$T(s) \approx gm_1 gm_s R_1 R_2 \cdot \frac{-s^2 \frac{C_c C_1}{2gm_B gm_s} + s \frac{C_c}{2gm_B} + 1}{(C_c C_1 C_c \frac{R_1 R_2}{gm_B}) s^3 + (C_1 R_1 R_2 (C_2 + C_c) s^2 + gm_s C_c R_1 R_2) s + 1}$$

- The common mode swing sets operating constraints for the input stage
- The output swing sets constraints for the operating point of the output stage
- SR, GBWP and E^2_{in} set constraints on the current of the input stage
- The gain sets constraints on the output transistor's length
- The offset sets constraints on the input transistor's length
- The noise corner sets constraints on the nMOS input transistor's length
- CMRR sets constraints on the length of the tail transistor

Root Locus Rules

- # BRANCHES = # POLES OF $G(s)$;
- Branches proceed from poles to zeros (finite or infinite);
- $\gamma < 0$ regions on the $\text{Re}[s]$ axis on the ~~right~~^{left} of an odd number of singularities;
- $\gamma > 0$ regions of the $\text{Re}[s]$ axis on the left side of an even number of singularities;
- # ASYMPTOTES = (#POLES) - (#ZEROES @ FINITE FREQUENCY)
- ASYMPTOTES = branches going to ∞ that always split the guess plane into even parts

Write the T.F. in the trans form.

The switched capacitor (SC) mimics the behavior of a large resistance, as it is widely used in filter design in audio range. We can make integrators based on a SC, who basically integrates current pulses, hence providing voltage steps at the output. The result is a staircase output waveform with an equivalent sample-rate

$$\frac{\Delta V}{T} = \frac{E \cdot C_1}{C} \cdot \frac{1}{T} = \frac{E}{C \cdot R_{eq}}$$

$$R_{eq} = \frac{I}{C_1}$$

The discrete approximation is good enough provided that the clock frequency is much larger than the BW of the input signal, hence it respects Shannon theorem. This can be easily done, since typical frequencies $\approx 17\text{Hz}$, while the audio range is $\approx 20\text{kHz}$ at the most.

We've already discussed the advantages, let's see now what's the bad part of dealing with discrete time systems:

we can write the output waveform like a staircase


$$v_{out}(t) = \sum_{m=0}^{+\infty} v_{out}(mT) \times \left\{ \text{rect} \left[\frac{t-mT}{T} \right] \right\}$$

where

$$\text{rect}(x) = \begin{cases} 1 & |x| < \frac{1}{2} \\ 0 & |x| > \frac{1}{2} \end{cases}$$

and
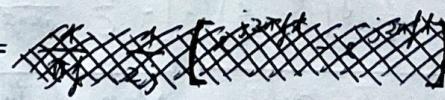
$$\mathcal{F} [\text{rect}(t)](f) = \int_{-\frac{1}{2}}^{\frac{1}{2}} e^{-j2\pi ft} dt = -\frac{1}{2\pi f j} \left[e^{-j2\pi ft} \right]_{-\frac{1}{2}}^{\frac{1}{2}} =$$



$$= \frac{1}{\pi f} \cdot \frac{1}{2j} \left[e^{j\pi f} - e^{-j\pi f} \right] = \frac{\sin(\pi f)}{\pi f} = \text{sinc}(f)$$

Let's see now what is the link between the Fourier transform of the continuous-time signal and the discrete-time one, from input to output:

$$\mathcal{F} [v_{in}(t)] = \sum_{m=0}^{+\infty} v_{in}(mT) \cdot \underbrace{e^{-j\pi mft} \text{sinc}\left(\frac{f}{f}\right) \cdot T}_{\mathcal{F} \left\{ \text{rect} \left[\frac{t-mT}{T} \right] \right\}} = \sum_{m=-\infty}^{+\infty} v_{in}(mT) z^{-m} \Big|_{z=e^{j2\pi f/T}} \cdot \text{TRC}(f)$$

ZETA TRANSFORM

(2) So we came to this result:


$$V_{\text{out}}(f) = V_{\text{in}}(z) \Big|_{z=e^{j2\pi fT}} \cdot T \text{ sinc}\left(\frac{f}{f}\right)$$

Now, from the circuit we have that

$$V_{\text{out}}(m+1) = V_{\text{out}}(m) - V_{\text{in}}(m) \frac{C_1}{C}$$

\Downarrow ZETA TRANSFORM
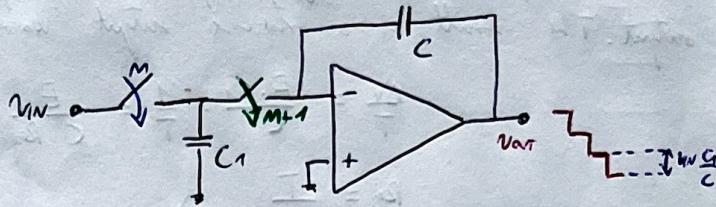
$$V_{\text{out}}(z) - V_{\text{out}}(1) = V_{\text{in}}(z) - V_{\text{in}}(z) \frac{C_1}{C}$$



$$\frac{V_{\text{out}}(z)}{V_{\text{in}}} = - \frac{C_1}{C} \frac{1}{z-1} = H(z) \Rightarrow \text{Transfer function of the discrete-time filter}$$

So we can write

$$V_{\text{out}}(f) = V_{\text{in}}(z) \cdot H(z) \Big|_{z=e^{j2\pi fT}} \cdot T \text{ sinc}\left(\frac{f}{f}\right)$$

where

$$\begin{aligned} V_{\text{in}}(z) \Big|_{z=e^{j2\pi fT}} &= \sum_{m=0}^{+\infty} v_{\text{in}}(mT) e^{-j2\pi fTm} = \int_{-\infty}^{+\infty} v_{\text{in}}(t) \cdot \sum_{m=0}^{+\infty} \delta(t-mT) e^{-j2\pi fTm} dt \\ &= \mathcal{F} \left[v_{\text{in}}(t) \sum_{m=0}^{+\infty} \delta(t-mT) \right] (f) \\ &= V_{\text{in}}(f) * \sum_{n=-\infty}^{+\infty} \frac{1}{T} \delta(f - \frac{n}{T}) \end{aligned}$$

and, in the end, we have

$$V_{\text{out}}(f) = \underbrace{\left[V_{\text{in}}(f) * \sum_{n=-\infty}^{+\infty} \frac{1}{T} \delta(f - \frac{n}{T}) \right]}_{\text{aliasing due to sampling}} \cdot \underbrace{\left[- \frac{C_1}{C} \frac{1}{e^{j2\pi fT} - 1} \right]}_{\text{action of the integrator, it is a passive filter}} \cdot \underbrace{\left[T \text{ sinc}\left(\frac{f}{f}\right) \right]}_{\text{spurious coded by the sampling}}$$

In order to have a reliable output, we need:

- a RECONSTRUCTION FILTER that kills all the HF harmonics due to aliasing;
- an ANTI-ALIASING FILTER before the the SC filter in order to kill MF distortions that may we brought to base-band due to aliasing;
- an EQUALIZING FILTER that compensates the spectrum shape alteration due to the windowing term.

All these filters can be easily implemented by continuous-time networks.